

# Novel strategies for high-granularity and radiation hardness LGAD sensors and front-end electronics


Michele CASELLE  
(KIT)  
[michele.caselle@kit.edu](mailto:michele.caselle@kit.edu)

KSEIT


# Readout chains
 
## What makes the different between normal sensor and fast sensor?

- Typical front-end readout chain for “slow” silicon sensor in High Energy Physics (HEP)



 - Front-end readout chain for “Fast” silicon detector in High Energy Physics (HEP)




- How can we enhance the time resolution?
- What are the key parameters influencing it?
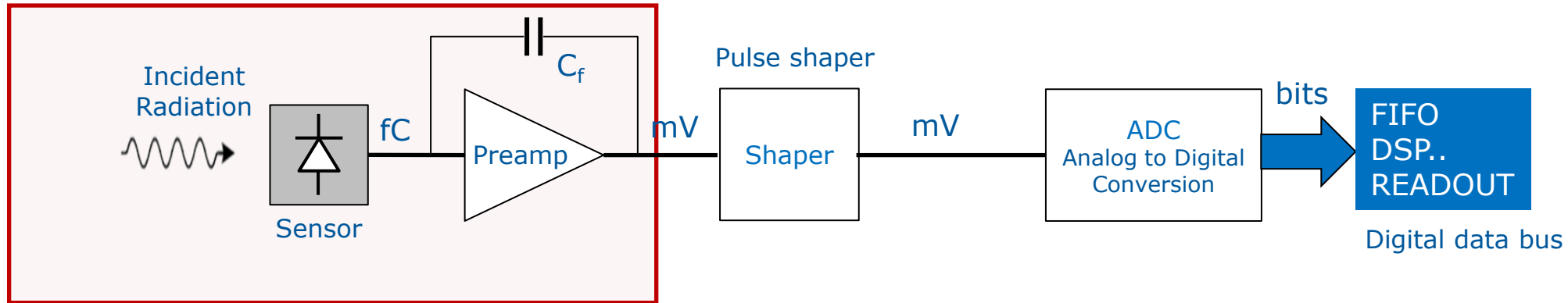
# Readout chains


What makes the different between normal sensor and fast sensor?

- Typical front-end readout chain for “slow” silicon sensor in High Energy Physics (HEP)


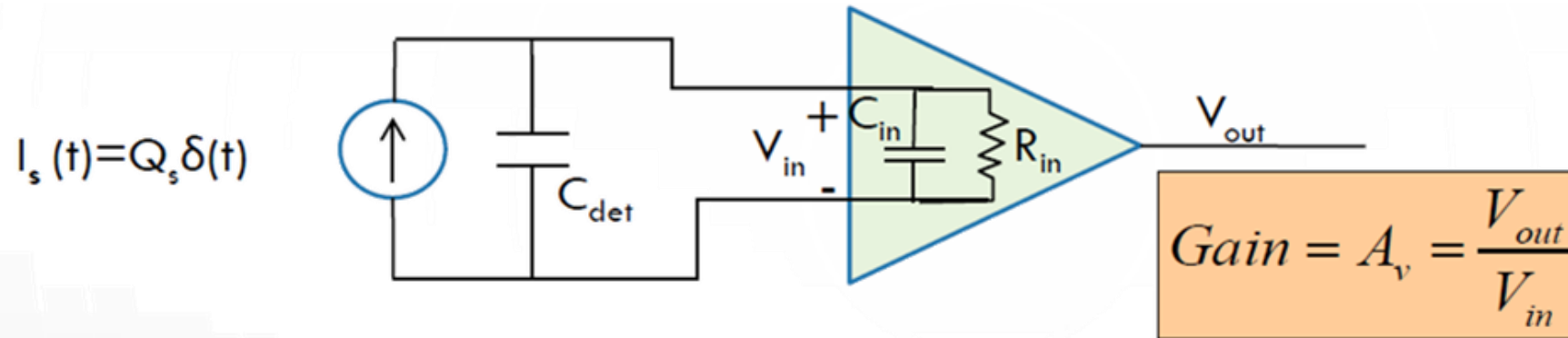
# Voltage with Capacitive Sources

What makes efficient the signal collection from silicon sensor?



- $R_{in}$  is usually very large (because physically connected to the gate of the input transistor)
- $I_s$  is integrated across the total capacitance  $C_T$

$$C_T = C_{det} + C_{in} \quad \longrightarrow \quad \begin{cases} V_{in} = \frac{1}{C_T} \int I_S(t) dt = \frac{Q_s}{C_{det} + C_{in}} \\ V_{OUT} = -A V_{in} = A \frac{Q_S}{C_{det} + C_{in}} \end{cases} \quad \begin{array}{l} V_{out} \text{ is proportional to } Q_s \\ \text{BUT ... it also depends on } C_{det}!!! \end{array}$$

- This is not desirable in the systems where  $C_{det}$  can vary different strip length/width, bias voltage, etc...


# Active integrator based on Charge Sensitive

Most used amplification stage for many sensors

- Inverting voltage amplifier:  $v_o = -A v_i$
- Input impedance:  $\infty$

$$Q_i = \int i_s(t) dt$$

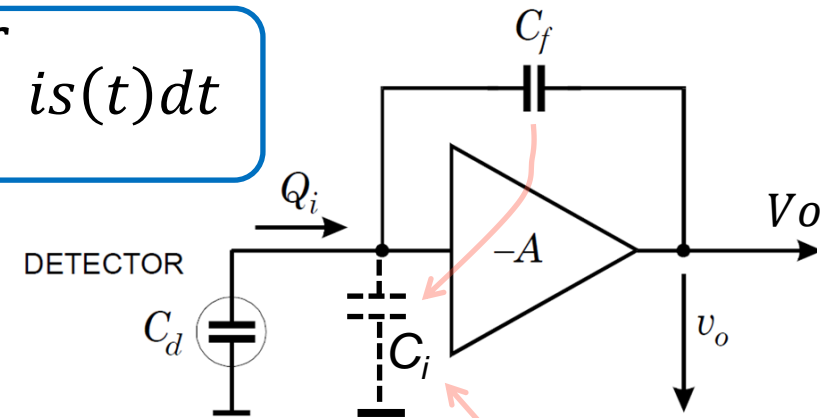- What is the effective input capacitance seen from the detector
- By Miller theorem, effective input capacitance  $C_i = C_f (1+A)$




Dynamic input capacitance

- Gain of the system:

$$A_Q = \frac{V_o}{Q_i} = \frac{A v_{in}}{C_i v_{in}} = \frac{A}{C_f (1 + A)} \cong \frac{1}{C_f} \text{ if } A \gg 1$$

 - Set by a well-controlled quantity, the feedback capacitance



- CSA is a pure integrator
- Dirac pulse  $\rightarrow$  step function

$$V_o = -\frac{1}{C_f} \int i_s(t) dt = -\frac{Q_i(t)}{C_f}$$


# Active integrator based on Charge Sensitive

Most used amplification stage for many sensors

- Inverting voltage amplifier:  $v_o = -A v_i$
- Input impedance:  $\infty$

$$Q_i = \int i_s(t) dt$$

 - What is the effective input capacitance seen from the detector
- By Miller theorem, effective input capacitance  $C_i = C_f (1+A)$



- Gain of the system:


$$v_{out}(t) = -a_0 v_{in}(t) = -\frac{1}{C_f} \int_0^t i_S dt' = -\frac{Q_S(t)}{C_f}$$

$$A_Q = \frac{V_o}{Q_i} = \frac{A v_i}{C_i v_i} = \frac{A}{C_f (1 + A)} \cong \frac{1}{C_f} \text{ if } A \gg 1$$

Dynamic input capacitance

*BUT ... not all the charge goes in the amplifier: a small fraction  $Q_{det}$  remains on  $C_{det}$  !!!*

 - Set by a well-controlled quantity, the feedback capacitance



- CSA is a pure integrator
- Dirac pulse  $\rightarrow$  step function

$$V_o = -\frac{1}{C_f} \int i_s(t) dt = -\frac{Q_i(t)}{C_f}$$

# Realistic Charge-Sensitive Preamplifiers

Amplifiers may be too slow to follow the instantaneous detector pulse


- Charge  $Q_s$  is divided across two capacitors  $C_{det}$  and  $C_{in}$
- What is the fraction of the charge that contributed to the  $V_o$  and what is the fraction that will not contribute because remain on the  $C_{det}$  ?

$$\frac{Q_{in}}{Q_s} = \frac{Q_{in}}{Q_{in} + Q_{det}} = \frac{1}{1 + \frac{Q_{det}}{Q_{in}}} = \frac{1}{1 + \frac{C_{det}}{C_{in}}}$$

- What is the value of  $C_{in}$  ?
- $C_i = C_f (1+A)$ , where  $A$  is the intrinsic voltage gain of the amplifier

$$\frac{Q_{in}}{Q_s} = \frac{Q_{in}}{Q_{in} + Q_{det}} = \frac{1}{1 + \frac{Q_{det}}{Q_{in}}} = \frac{1}{1 + \frac{C_{det}}{C_f (1 + A)}}$$

- **Voltage gain “A” play an important role in the charge collection & efficiency**
- Example:  $C_{det} = 160 \text{ fF}$ ,  $A = 10^2$ ,  $C_f = 16 \text{ pF}$ , the fraction of the charge collected is:  $Q_{in}/Q_s = 0.9 \rightarrow$  **10 % lost**
- $C_{det} = 160 \text{ fF}$ ,  $A = 10^3$ ,  $C_f = 16 \text{ pF}$ , the fraction of the charge collected is:  $Q_{in}/Q_s = 0.99 \rightarrow$  **1 % lost**

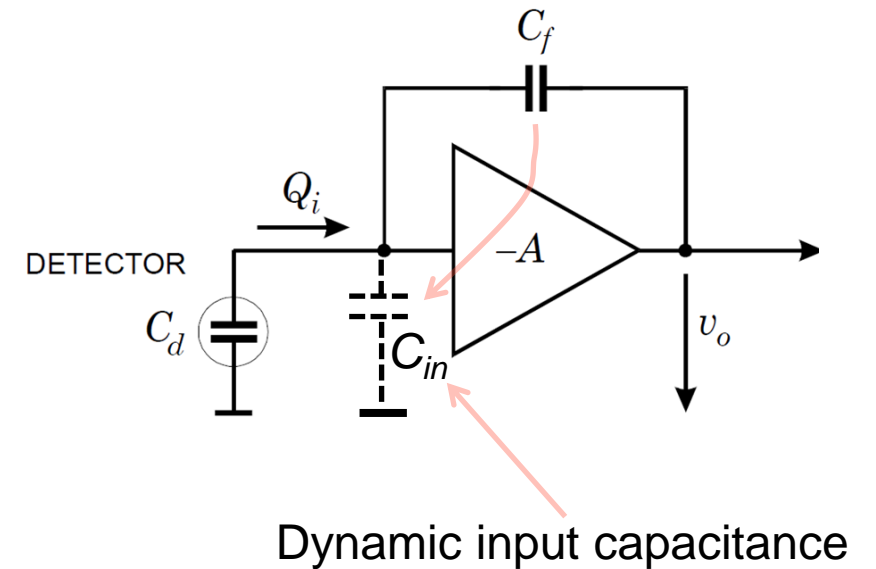

# Realistic Charge-Sensitive Preamplifiers

Amplifiers may be too slow to follow the instantaneous detector pulse

- Charge  $Q_s$  is divided across two capacitors  $C_{det}$  and  $C_{in}$
- What is the fraction of the charge that contributed to the  $V_o$  and what is the fraction that will not contribute because remain on the  $C_{det}$  ?

$$\frac{Q_{in}}{Q_s} = \frac{Q_{in}}{Q_{in} + Q_{det}} = \frac{1}{1 + \frac{Q_{det}}{Q_{in}}} = \frac{1}{1 + \frac{C_{det}}{C_{in}}}$$


- What is the value of  $C_{in}$  ?
- $C_i = C_f (1+A)$ , where  $A$  is the intrinsic voltage gain of the amplifier

$$\frac{Q_{in}}{Q_s} = \frac{Q_{in}}{Q_{in} + Q_{det}} = \frac{1}{1 + \frac{Q_{det}}{Q_{in}}} = \frac{1}{1 + \frac{C_{det}}{C_f (1+A)}}$$

- Voltage gain “ $A$ ” play an important role in the charge collection & efficiency

 - Example:  $C_{det} = 160$  fF,  $A = 10^2$   $C_f = 16$  pF, the fraction of the charge collected is:  $Q_{in}/Q_s = 0.9 \rightarrow$  **10 % lost**

- $C_{det} = 160$  fF,  $A = 10^3$   $C_f = 16$  pF, the fraction of the charge collected is:  $Q_{in}/Q_s = 0.99 \rightarrow$  **1 % lost**



Dynamic input capacitance


*BUT ... we are considering an ideal amplifier with infinite bandwidth (infinite speed) !!!*


 
# Realistic Charge-Sensitive Preamplifiers

Amplifiers may be too slow to follow the instantaneous detector pulse

- A pulse Dirac of input current  $\rightarrow$  generates a voltage step at the output of the CSA (if  $\infty$  bandwidth (BW))




$$V_o = -Q_{in} \int i_s(t) dt = -\frac{Q_{in}}{C_f}$$


- In reality, the voltage amplifier is dominated by its **dominant pole** (time constant) due to the internal capacitances in the amplifier must first charge up
 
# Realistic Charge-Sensitive Preamplifiers

Amplifiers may be too slow to follow the instantaneous detector pulse



FREQUENCY DOMAIN

 


UPPER CUTOFF FREQUENCY  $2\pi f_u$

$$\frac{1}{Z_L} = \frac{1}{R_L} + i\omega C_o \quad \text{Because } R_L \text{ is in parallel to } C_o$$

$$A_v = \frac{dv_o}{dv_i} = \frac{di_o}{dv_i} \cdot Z_L \equiv g_m Z_L \quad \text{Transconductance} = \frac{di_o}{dv_i} = g_m$$

TIME DOMAIN

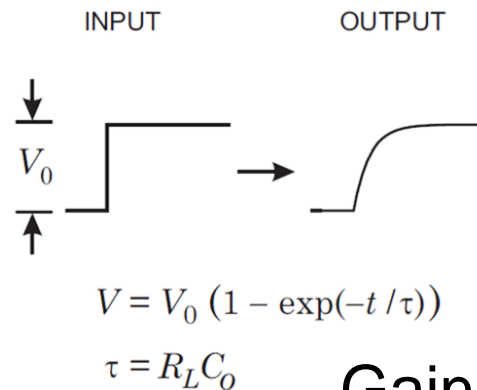

$$A(\omega) = \frac{A_0}{1 + i \frac{\omega}{\omega_0}} = \frac{g_m R_L}{1 + i \frac{\omega}{\omega_0}} \quad \text{where } \omega_0 = 1/\tau = 1/R_L C_o$$

low-frequency =  $g_m R_L$


high-frequency  $A(\omega) = -i A_0 \frac{\omega_0}{\omega}$

Gain-bandwidth product  $GBW = g_m R_L \frac{1}{R_L C_o} = \frac{g_m}{C_o}$

Detector capacitance  $\rightarrow$  IPE

# Realistic Charge-Sensitive Preamplifiers

For timing

 

Dynamic input capacitance


- Effective input capacitance  $C_i = C_f (1+A(\omega))$

- Input impedance  $Z_{in} = \frac{1}{i\omega C_i} \quad \omega \gg \omega_0$

- High frequency  $A(\omega) = -iA_0 \frac{\omega_0}{\omega}$

- Input impedance  $Z_{in} = \frac{1}{i\omega C_i} = \frac{1}{i\omega C_f (-iA_0 \frac{\omega_0}{\omega})} = \frac{1}{C_f A_0 \omega_0} = \frac{C_o}{C_f g_m}$

 
Depending on the size W/L of the input device



The input impedance of the CSA behaves as a resistor

Timing  $\tau_{CSA} = C_D Z_{in} = \frac{C_D}{C_f A_0 \omega_0} = \frac{C_D}{C_f} \frac{C_o}{g_m}$

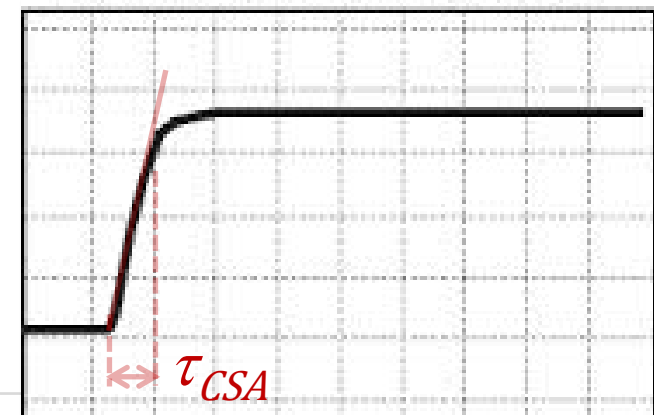Depends on the  $C_D$  and  $BW$  and  $g_m$  (power)




$V_{out}(t)$ : CSP output pulse: 10ns/div


# Realistic Charge-Sensitive Preamplifiers

## Discharging the $C_f$ and reset

ideal situation w/o reset

 

(a) Circuit diagram.

 


(b) Output voltage.


=> "pile-up" => saturation

- Reset circuit is necessary to discharge the  $C_f$


discharging options

 


(a) Switch reset: circuit.

 



(b) Switch reset: output voltage.

 

(c) Reset via resistor: circuit.

 

(d) Reset via resistor: output voltage.

  

"reset" switch

- Mainly employed for photon sciences, i.e. Kalypso detector system

resistor  $R_f$

- Very simple option, mainly employed for fast detector, i.e. timing detectors


a current source

- Very accurate option, many HEP front-end, i.e. ATLAS, CMS, etc.
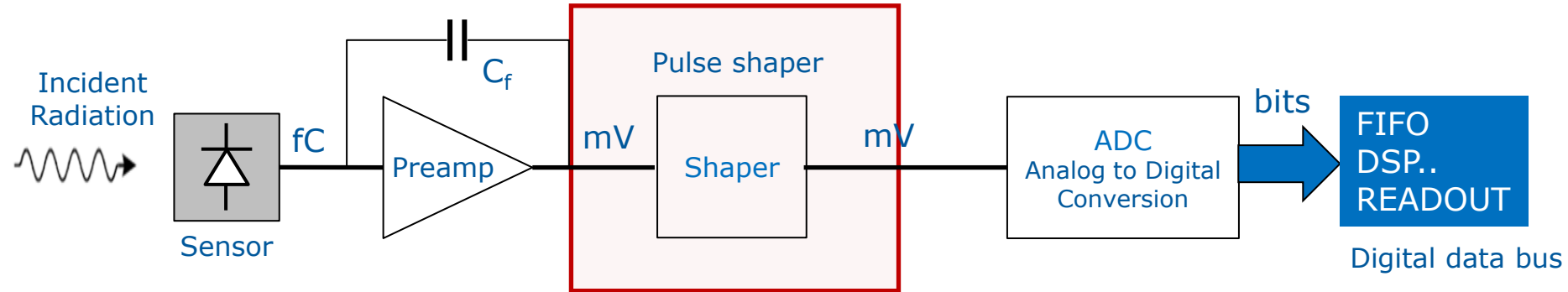
# Readout chains

What makes the different between normal sensor and fast sensor?


- Typical front-end readout chain for “slow” silicon sensor in High Energy Physics (HEP)



# Pulse shaping

 
## Semi-Gaussian filter based on CR-(RC)<sup>M</sup> filter (shaper)

- To reduce the noise generated from the sensor (short noise) and the CSA (thermal noise) before the ADC conversion



High-pass filter

$$H_1(s) = \frac{sRC}{1 + sRC}$$

 

Low-pass filter


$$H_2(s) = \frac{1}{1 + sRC}$$

- What are the main characteristics of the shaper?
- How does the peaking time factor in?

# Pulse shaping
 
## Semi-Gaussian filter based on CR-(RC)<sup>M</sup> filter (shaper)

- To reduce the noise generated from the sensor (short noise) and the CSA (thermal noise) before the ADC conversion




In the time domain  $V_{sh}(t) = A \frac{t}{\tau} e^{-\frac{t}{\tau}}$

- $A = \text{pulse amplitude} = \frac{Q_i(t)}{C_f}$



 
- The peaking time is always at  $t=\tau$  independently on the pulse amplitude (energy released into sensor)
- Where  $\tau = RC$



- This is called CR-(RC)<sup>M</sup>

- $V_{sh}(t) = A \frac{1}{M!} \left(\frac{t}{\tau}\right)^M e^{-\frac{t}{\tau}}$


 
- To improve the pile-up of the signal (see next slide)
- To increase the bandwidth → less noise reduction




# Pulse shaping vs pileup
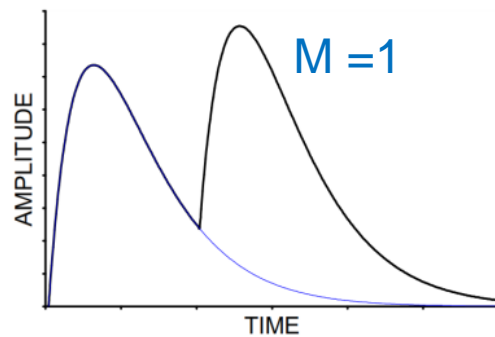 
## Semi-Gaussian filter based on CR-(RC)<sup>M</sup> filter (shaper)

- To reduce the noise generated from the sensor (short noise) and the CSA (thermal noise) before the ADC conversion



Pile-up

 


No pile-up

- Improve S/N ratio → restrict bandwidth → increase pulse width

- But increase the pile-up

- Reduce the pile-up → decrease pulse width

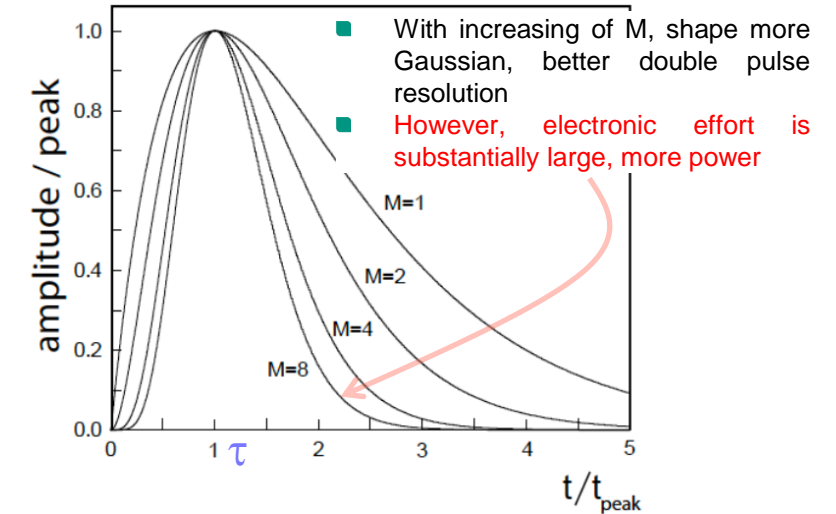- Reduce S/N ratio, more complex, more power




- Two conflicting objectives arise: the optimal filter depends on the specific physics application and the pixel or channel geometry of the sensor




# Some more things ...

## “Ballistic deficit” or “shaping loss”

 

 - The term "ballistic deficit" refers to a phenomenon in particle detectors, particularly in systems using charge-sensitive amplifiers and shaping circuits, where the **signal's amplitude is reduced due to incomplete charge collection within the shaping time**. This effect can significantly impact the accuracy of energy measurements in detectors




- If signal step at the output of CSA takes much longer than the shaper  $\tau_{CR}$
- caused e.g.
  - by a large charge collection time
  - by a large input capacitance
  - by an intrinsically slow preamplifier
- The  $V_{out}$  (shaper) is trimmed by the slow rise of the preamplifier output pulse
- **Mitigation strategies, include:** Optimizing Shaping Time, designing detectors with uniform and fast charge collection properties, such as using high-field regions to speed up carrier drift, understanding the detector's response through simulations and measurements to anticipate and compensate for ballistic deficit effects


# What about the peaking time?

Fast shaper  $\rightarrow$  ballistic deficit


f(t) Current from sensor

 

h(t) Shaper delta response

 

v(t) Vout shaper

 


Source: Werner Riegler, CERN


# Readout chains
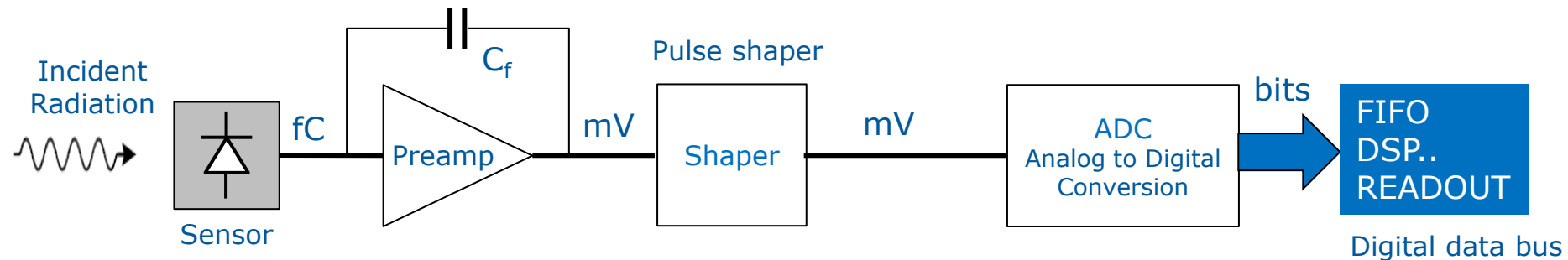
## What makes the different between normal sensor and fast sensor?

- Typical front-end readout chain for “slow” silicon sensor in High Energy Physics (HEP)



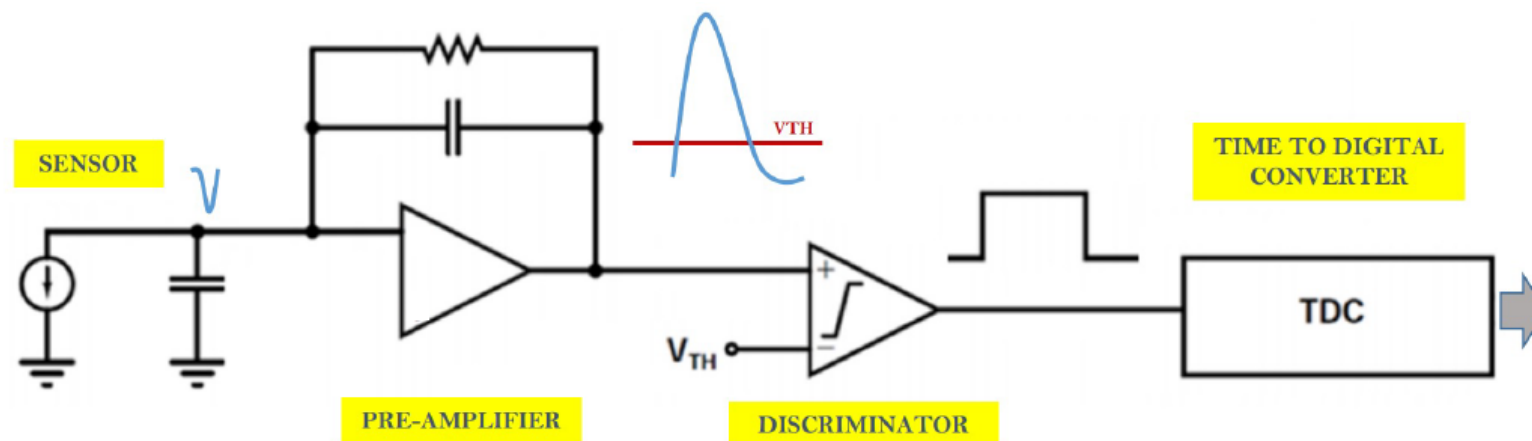
- Front-end readout chain for “Fast” silicon detector in High Energy Physics (HEP)



- How can we improve the time resolution?
- What are the key parameters ?
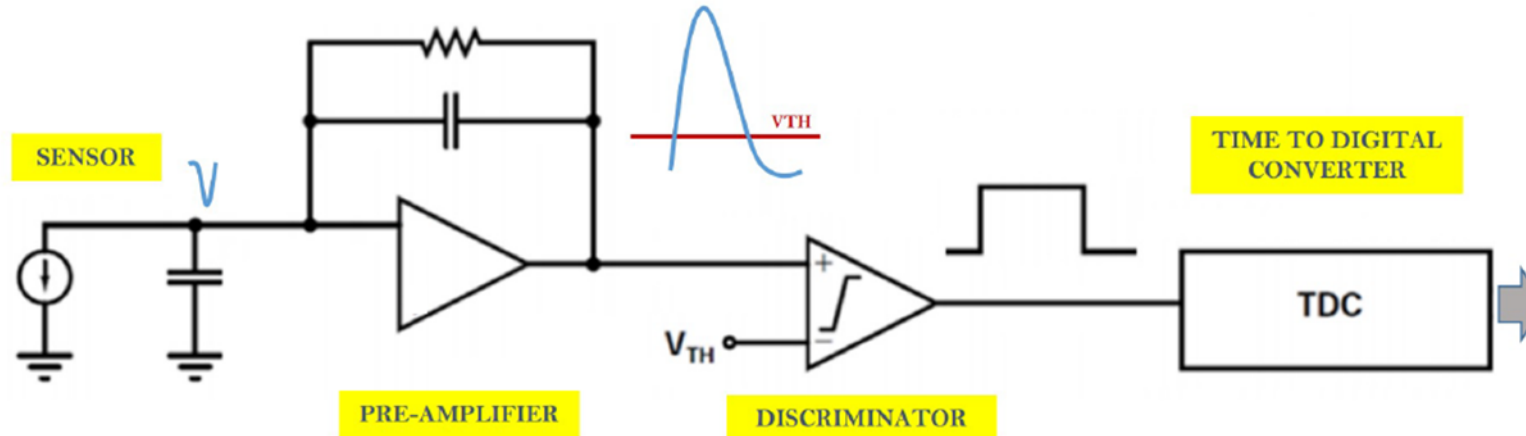
# Readout chains of fast silicon sensors

What makes the different between normal sensor and fast sensor?



## ■ Readout chain consists of:


- Preamplifier (first stage, the noise strongly depend on this stage)
- Fast comparator
- High resolution TDC

# Time resolution in timing detectors

The timing capabilities depends on the signal at the output of the pre-amplifier and by the TDC binning

■ Timing measurements is limited by:

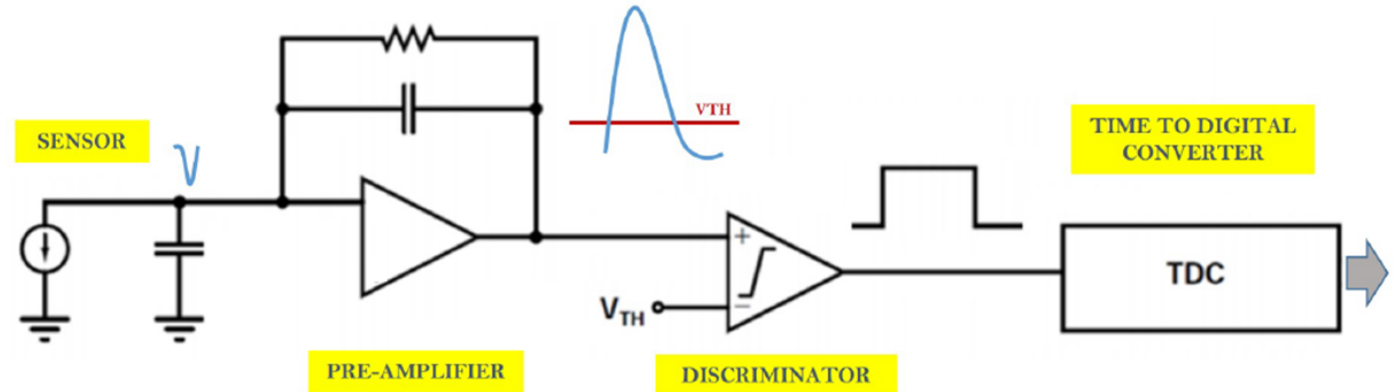- **Jitter** → timing resolution
- **Time walk** → timing accuracy




$$\sigma_t^2 = \underbrace{\left(\frac{\text{Noise}}{dV/dt}\right)^2 + \sigma_{timewalk}^2}_{\text{Front-end}} + \underbrace{\left(\frac{\text{LSB}}{\sqrt{12}}\right)^2}_{\text{TDC}} + \underbrace{\sigma_{sensor}^2 + \sigma_{Landau}^2}_{\text{Sensor}}$$

**Total noise contribution**
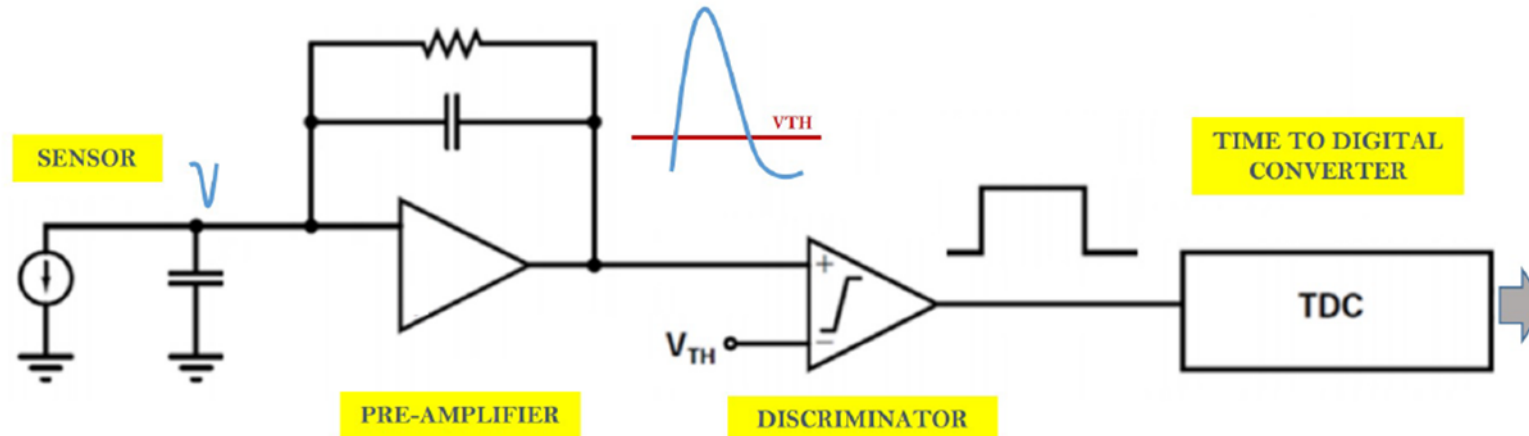
# Time resolution in timing detectors

The timing capabilities depends on the signal at the output of the pre-amplifier and by the TDC binning



$$\sigma_t^2 = \underbrace{\left(\frac{\text{Noise}}{dV/dt}\right)^2 + \sigma_{timewalk}^2}_{\text{Front-end}} + \underbrace{\left(\frac{\text{LSB}}{\sqrt{12}}\right)^2}_{\text{TDC}} + \underbrace{\sigma_{sensor}^2 + \sigma_{Landau}^2}_{\text{Sensor}}$$

## Total noise contribution

Yesterday lecture


- $\sigma_{Landau}^2$  → non-uniform energy deposition
  - Thinner sensor operating  $E_{sat}$  condition, reduce this noise contribution
- $\sigma_{sensor}^2$  → Weighting field and SNR
  - LGAD or 3D technologies, etc.

# Time resolution in timing detectors

The timing capabilities depends on the signal at the output of the pre-amplifier and by the TDC binning

■ Timing measurements is limited by:

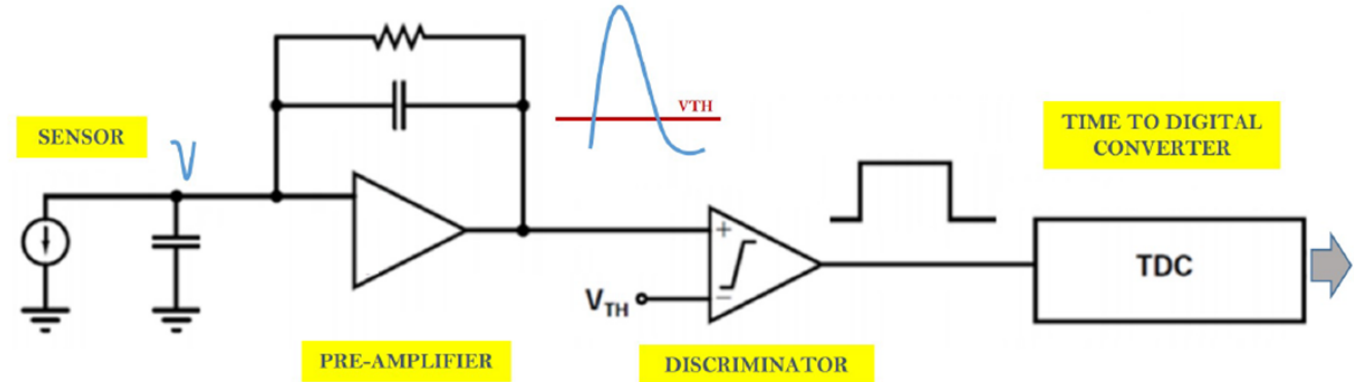- **Jitter** → timing resolution
- **Time walk** → timing accuracy



$$\sigma_t^2 = \underbrace{\left(\frac{\text{Noise}}{dV/dt}\right)^2 + \sigma_{timewalk}^2}_{\text{Front-end}} + \underbrace{\left(\frac{LSB}{\sqrt{12}}\right)^2 + \sigma_{sensor}^2 + \sigma_{Landau}^2}_{\text{Sensor}} + \sigma_{TDC}^2$$

## Total noise contribution


- **Noise:** There are two primary sources of noise—sensor noise (shot noise) and thermal noise from the electronics.
- **dV/dt:** This is influenced by several factors, including the sensor characteristics, signal speed, the open-loop gain of the charge-sensitive amplifier (CSA), bandwidth, and other parameters.
- **Time walk:** This effect is tied to the subsequent stage, which is based on the discriminator.

# Time resolution in timing detectors

The timing capabilities depends from the signal at the output of the pre-amplifier and by the TDC binning

■ Timing measurements is limited by:

 - **Jitter** → timing resolution
- **Time walk** → timing accuracy



$$\sigma_t^2 = \underbrace{\left(\frac{\text{Noise}}{dV/dt}\right)^2 + \sigma_{timewalk}^2}_{\text{Front-end}} + \underbrace{\left(\frac{LSB}{\sqrt{12}}\right)^2 + \sigma_{sensor}^2 + \sigma_{Landau}^2}_{\text{Sensor}} + \sigma_{TDC}^2$$

## Total noise contribution



- **Noise:** There are two primary sources of noise—sensor noise (shot noise) and thermal noise from the electronics.
- **dV/dt:** This is influenced by several factors, including the sensor characteristics, signal speed, the open-loop gain of the charge-sensitive amplifier (CSA), bandwidth, and other parameters.
- **Time walk:** This effect is tied to the subsequent stage, which is based on the discriminator.



# The jitter
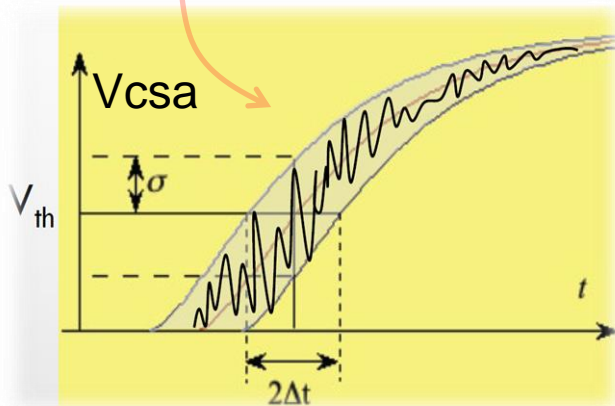 
## Noise has an impact in the time measurements

- Uncertainty in the time of crossing threshold  $\rightarrow$  *jitter*



- $\Delta t = \frac{\sigma_{noise}}{dV/dt}$

Sensor + electronics noise

Slope of the signal (Timing  $\tau_{CSA}$ )

$$\text{Timing } \tau_{CSA} = \frac{C_D}{C_f A_0 \omega_0} = \frac{C_D}{C_f} \frac{C_o}{g_m}$$

Annotations: Gain points to  $A_0$ , Bandwidth points to  $\omega_0$ , Power points to  $g_m$ .

- How to decrease jitter?

Conflicting conditions:

- Decrease  $\sigma_{noise}$   $\rightarrow$  decrease bandwidth
- Increase slope  $\rightarrow$  increase bandwidth

- Increasing the  $A_0$  the open loop gain  $\rightarrow$  more power, more complex


- LGADs (Low Gain Avalanche Detectors) offer a significant combined with very short charge collection times and relatively low noise levels. As a result, LGADs are a key sensor technology for addressing the conflicting requirements often encountered with traditional sensors, providing an optimal balance between speed, sensitivity, and noise performance

# Time resolution in timing detectors

The timing capabilities depends from the signal at the output of the pre-amplifier and by the TDC binning

■ Timing measurements is limited by:

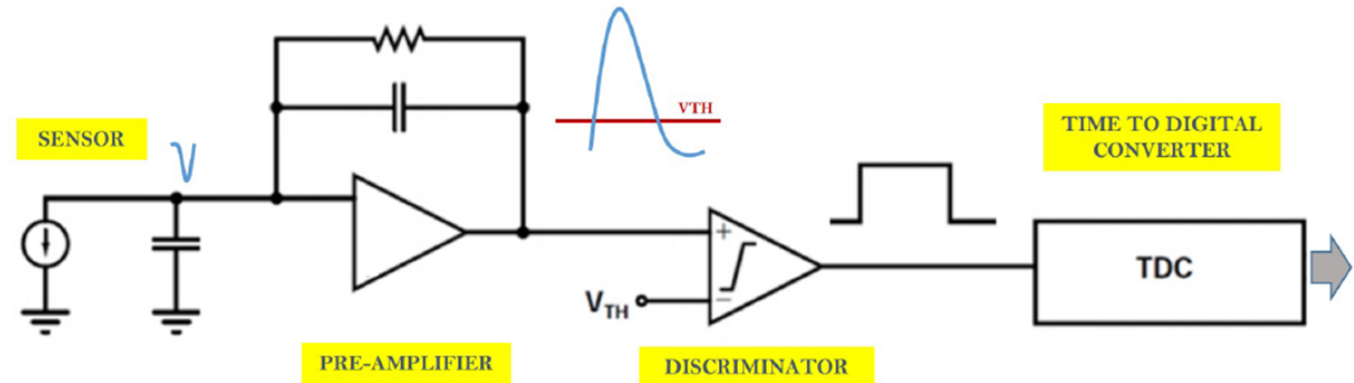- **Jitter** → timing resolution
- **Time walk** → timing accuracy



$$\sigma_t^2 = \underbrace{\left(\frac{\text{Noise}}{dV/dt}\right)^2 + \sigma_{timewalk}^2}_{\text{Front-end}} + \underbrace{\left(\frac{LSB}{\sqrt{12}}\right)^2 + \sigma_{sensor}^2 + \sigma_{Landau}^2}_{\text{Sensor}} + \text{TDC}$$



## Total noise contribution

- **Noise:** There are two primary sources of noise—sensor noise (shot noise) and thermal noise from the electronics.
- **dV/dt:** This is influenced by several factors, including the sensor characteristics, signal speed, the open-loop gain of the charge-sensitive amplifier (CSA), bandwidth, and other parameters.
- **Time walk:** This effect is tied to the subsequent stage, which is based on the discriminator.

# Time measurements
 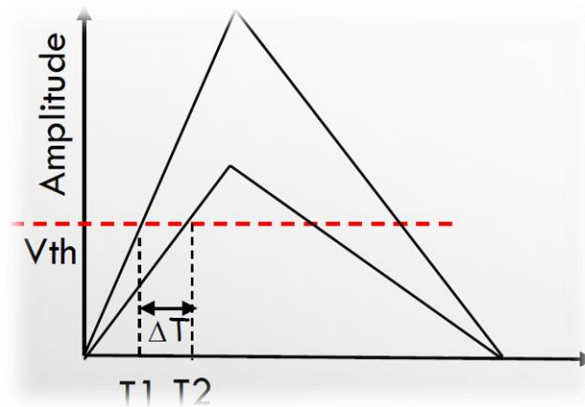
## Time walk from standard leading edge discriminator

- The simplest scheme is based on: Leading edge or Threshold discriminator (comparator), when the signal crosses a threshold, the output goes from “low” to “high” level
- In the leading edge discriminators, two pulses with identical shape and time of occurrence, but different amplitude cross the same threshold in different times: **amplitude time walk**
- Even if the input amplitude is constant, time walk can still occur if the shape (rise time) of the pulse changes (for example, for changes in the charge collection time): **rise time walk**




- The sensitivity of leading edge discriminator to time walk is minimized by setting the threshold *as low as possible* but it must be compatible with noise level
- Time walk correction:
  - By time-over-threshold ToT: measure the pulse amplitude and apply correction to timing
  - Hardware: employ the crossover timing, Constant Fraction timing


# Time walk correction
 
## Crossover timing and Constant Fraction timing

- The crossover timing can greatly reduce the magnitude of the amplitude time walk
- *Hypothesis*: the output of the shaper is a bipolar pulse, and the time of zero-crossing is independent of the pulse amplitude



 - If the output of shaper is unipolar, but the peaking time is constant, adding a differentiator (C-R network) we get a bipolar pulse crossing the zero in correspondence of the signal peak



As a derivation function



- This method reduce amplitude time walk, but *usually jitter is larger* than leading edge triggering

Improve the timing accuracy

reduce the timing resolution

# Time walk correction

## Constant Fraction timing

 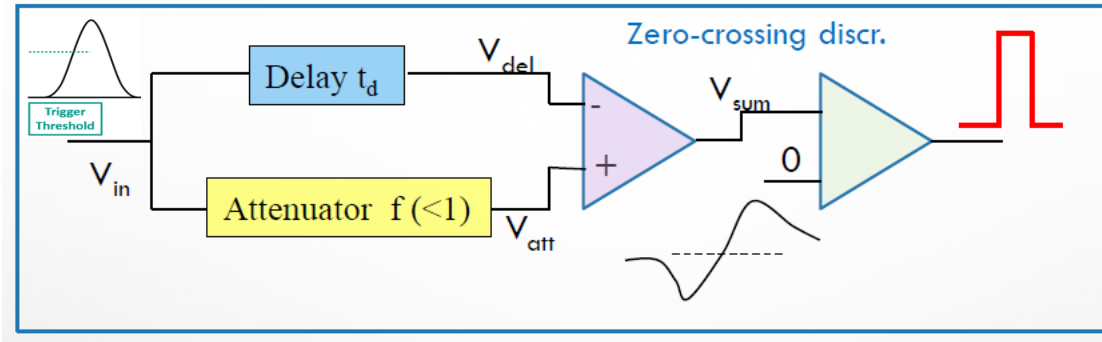


- Summing:
  - inverted and delayed signal, with  $t_d > t_{rise}$
  - attenuated signal
- It can be demonstrated that the Constant Fraction Discriminator (CFD) time of resulting bipolar signal is independent of pulse amplitude for all pulses with constant shape
- Resulting jitter for optimal parameters ( $t_d$ ,  $f$ ) is lower than cross-over discriminator technique

high the timing accuracy

high the timing resolution
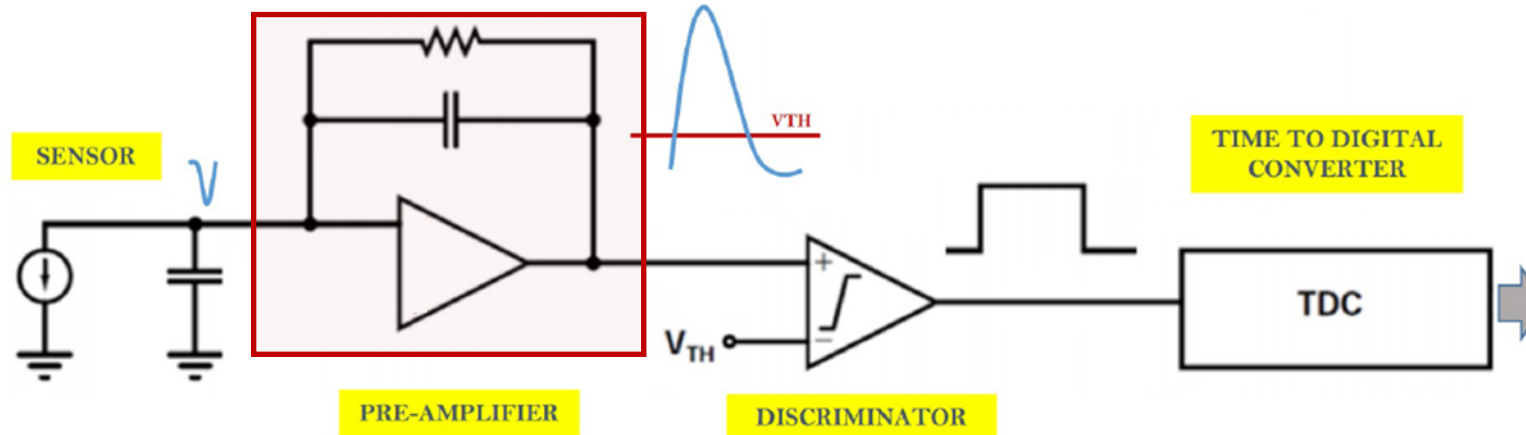
# Readout chains of fast silicon sensors

What makes the different between normal sensor and fast sensor?



## ■ Readout chain consists of:


- Preamplifier (first stage, the noise strongly depend from this stage)
- Fast comparator
- High resolution TDC

# What is the best preamplifier devices

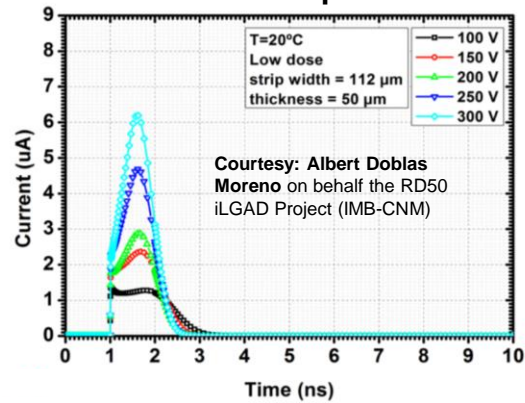
## Charge Sensitive vs Transimpedance Amplifier

- For planar silicon sensors, the charge collected consists of a limited number of carriers over a period longer than 10 ns, resulting in a very low associated current. Consequently, a Charge-Sensitive Amplifier (CSA) is essential for signal processing.
- In contrast, LGAD sensors generate a significantly larger charge signal over a much shorter time ( $\sim 1$  ns) compared to the  $>10$  ns typical of standard pixel or monolithic sensors. As a result, the associated signal is a fast current pulse


TCAD Simulation 50  $\mu\text{m}$  thick LGAD



■ From ...

 

■ To ...

 


# What is the best preamplifier devices


## Charge Sensitive vs Transimpedance Amplifier

- For planar silicon sensors, the charge collected consists of a limited number of carriers over a period longer than 10 ns, resulting in a very low associated current. Consequently, a Charge-Sensitive Amplifier (CSA) is essential for signal processing.
- In contrast, LGAD sensors generate a significantly larger charge signal over a much shorter time (~1 ns) compared to the >10 ns typical of standard pixel or monolithic sensors. As a result, the associated signal is a fast current pulse


TCAD Simulation 50 μm thick LGAD

 


■ From ...

 

■ To ...

 

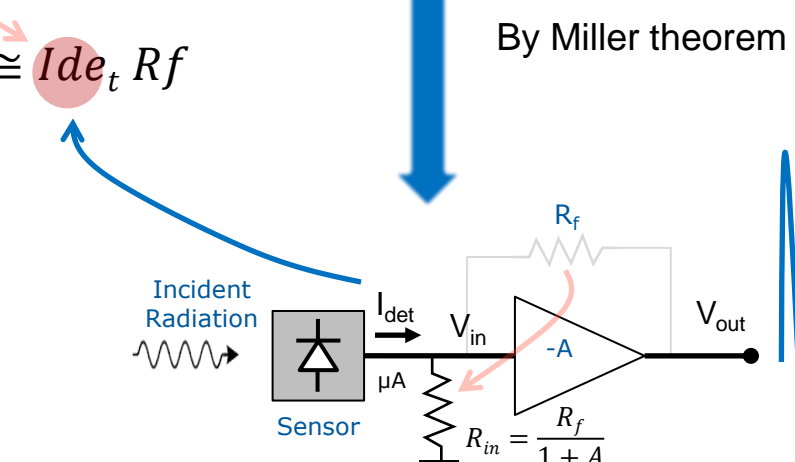■  $V_{out} = -A V_{in} = -A I_{det} * R_{in} = -A I_{det} \frac{R_f}{1+A} \cong I_{det} R_f$



By Miller theorem




# What is the best preamplifier devices


## Charge Sensitive vs Transimpedance Amplifier

- For planar silicon sensors, the charge collected consists of a limited number of carriers over a period longer than 10 ns, resulting in a very low associated current. Consequently, a Charge-Sensitive Amplifier (CSA) is essential for signal processing.
- In contrast, LGAD sensors generate a significantly larger charge signal over a much shorter time (~1 ns) compared to the >10 ns typical of standard pixel or monolithic sensors. As a result, the associated signal is a fast current pulse


TCAD Simulation 50 μm thick LGAD

 

From ...

 


To ...

 

$$V_{out} = -A V_{in} = -A I_{det} * R_{in} = -A I_{det} \frac{R_f}{1+A} \cong I_{det} R_f$$


By Miller theorem

- The **gain of a transimpedance amplifier is determined directly by the feedback resistor  $R_f$** . For example if the gain is = 80 dB  $\rightarrow R_f = 10 \text{ k}\Omega$  resulting in an output voltage  $V_{out}=60 \text{ mV}$ , requiring additional power
- The **input impedance  $R_{in} = R_f / (1+A)$** , for an open-loop gain  $A = 40 \text{ dB}$  ( $A=1000$ ),  $R_{in} \sim 10 \Omega$
- The **time constant** =  $\tau = C_{det} * R_{in}$  = is therefore very small, leading to extremely fast pulse response times with a steeper slope.

 




# What is the best preamplifier devices

## Why not both together ?

 


- The gain of the circuit is determined by the feedback capacitance  $C_f$ , similar to a Charge-Sensitive Amplifier (CSA). Specifically,  $V_{out} = Q_{in}/C_f$ , where  $C_f$  is typically in the femtofarad range.
- The feedback resistor  $R_f$  is used to shape the pulse width and is usually in the range of a few  $k\Omega$
- Enable a simple feedback mechanism for charge resetting, and the main amplifier design remains relatively uncomplicated

   - TOFFEE: a Fully Custom Amplifier-comparator Chip for Silicon Detectors with Internal Gain <https://ieeexplore.ieee.org/stamp/stamp.jsp?tp=&arnumber=8069854>


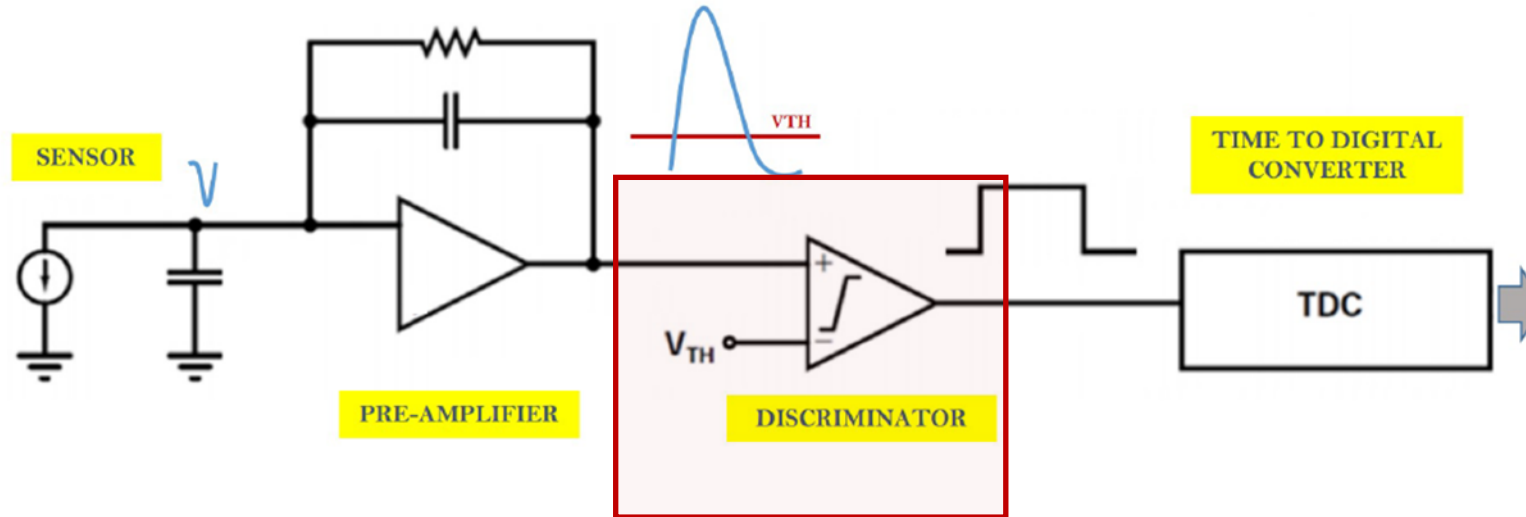
# Readout chains of fast silicon sensors

What makes the different between normal sensor and fast sensor?




## ■ Readout chain consists of:

- Preamplifier (first stage, the noise strongly depend from this stage)
- Fast comparator
- High resolution TDC

# Comparator architecture overview
 
## Applications of comparators


- **Basic building block of an A/D converter**
- Output amplifies difference between  $V_{IN}$  &  $V_{REF}$  with a large gain, output is 'digital' at either the positive or negative supply rail





# Introduction to the comparator
 
## What is a Comparator?

- The comparator is essentially a 1-bit analog-digital converter
  - Input is analog
  - Output is digital
- The comparator output is binary with the two-level outputs:
  - $V_{OH}$  = the high output of the comparator
  - $V_{OL}$  = the low level output of the comparator
- Circuit symbol for a comparator




## Voltage transfer function

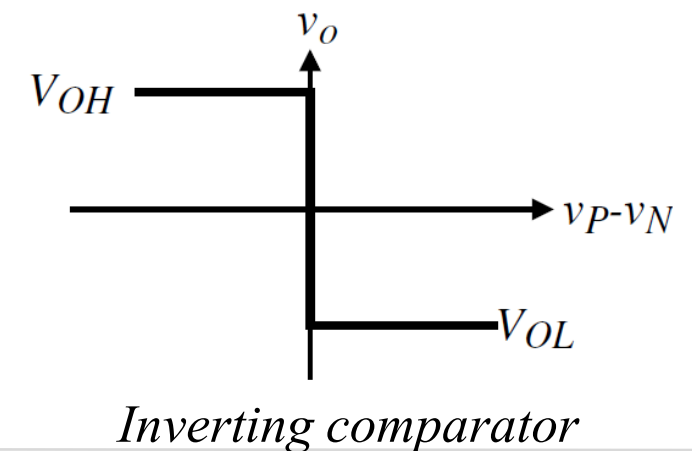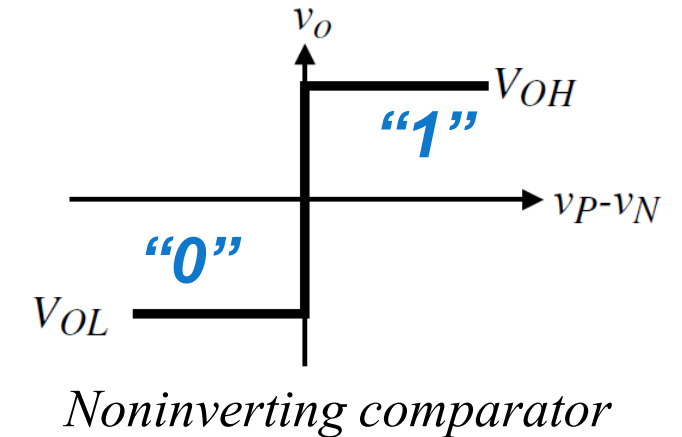


# Static characteristics
 
## “Ideal” and “real” transfer curves

- **Ideal comparator** the output changes states for an input  $\Delta V$  that approaches zero, which implies a gain of infinity





Model of Noninverting comparator

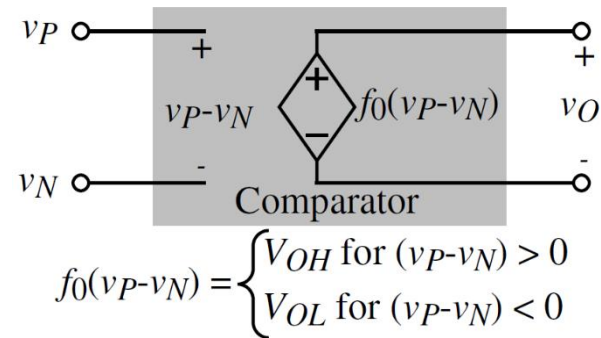

$$\text{Gain} = A_v = \lim_{\Delta V \rightarrow 0} \frac{V_{OH} - V_{OL}}{\Delta V}$$

where  $\Delta V$  is the input voltage

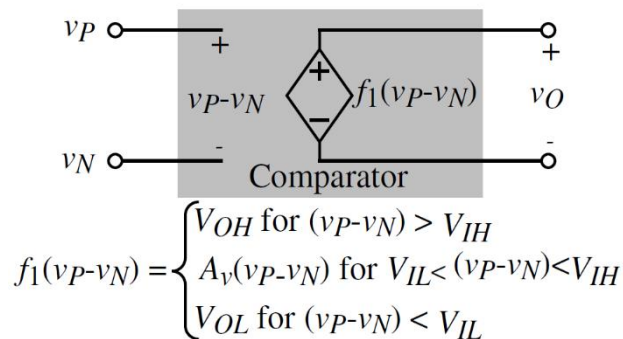 - First **nonideal** effect of comparator is a **limited** gain  $A_v$




$$\text{Voltage gain is: } A_v = \frac{V_{OH} - V_{OL}}{V_{IH} - V_{IL}}$$

■ **DEF:** The minimum amount on input voltage necessary to make the output swing between two binary states is defined: **resolution of the comparator**

# Dynamic characteristics
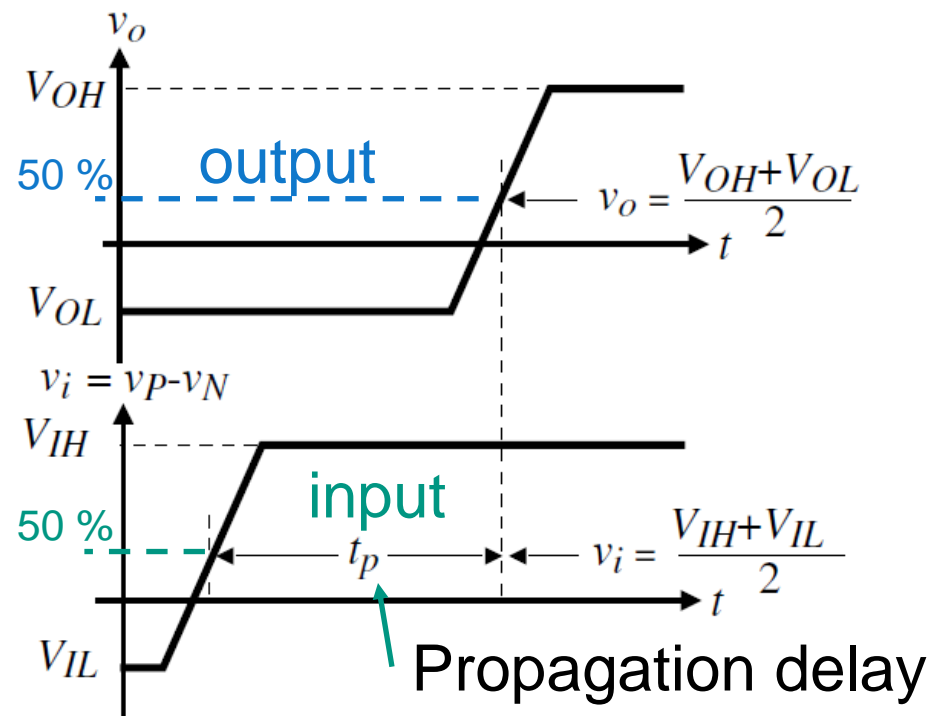
## Propagation delay time

- The delay between the input analog signal and digital output response of the comparator is defined **propagation delay time**
- The propagation delay is very important because limits the conversion speed rate of an A/D converters




- The propagation delay generally varies as function of the amplitude of the input
- Large input  $\rightarrow$  smaller delay time
- Propagation delay **is large** when the comparator operates in **small-signal mode** and **smaller** when operates in **slew-rate mode**
- The comparator operates in **slewing** or **slew-rate** when further increase in the input will not long effect the delay propagation delay

# Two-stage, open-loop comparators
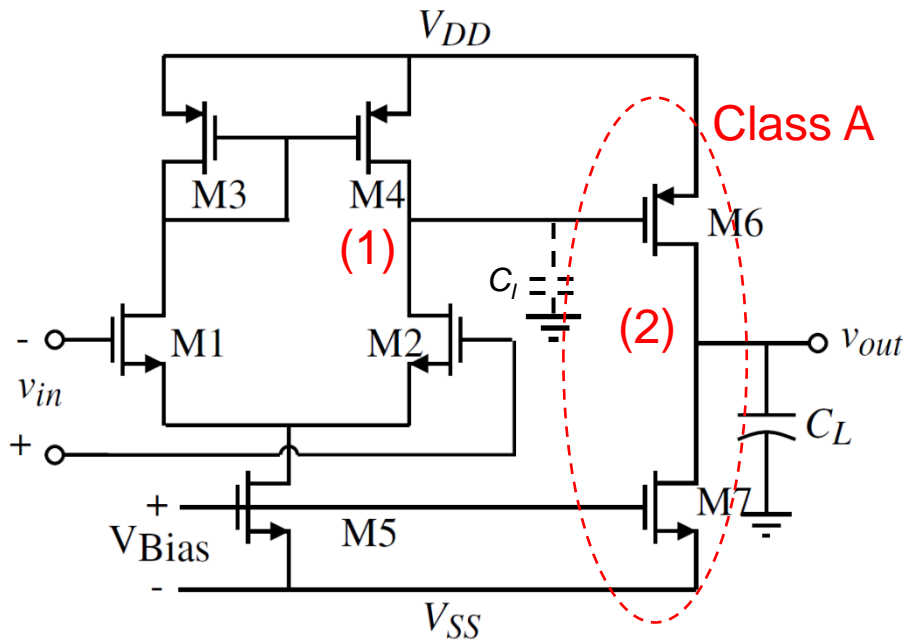
## Propagation delay time

- The comparator requires: differential input a high-gain to be able to achieve the desired resolution, the two-stage op amp makes an excellent implementation of the comparator



- The comparator generally works in open-loop mode, therefore it is not necessary any compensation capacitance → it is **preferable not compensate so that it has a large bandwidth possible**

- The small-signal voltage gain:  $A_v(0) = \underbrace{\left( \frac{g_{m1}}{g_{ds2} + g_{ds4}} \right)}_{(1)} \underbrace{\left( \frac{g_{m6}}{g_{ds6} + g_{ds7}} \right)}_{(2)}$
- The poles are:

$$p_1 = \frac{-(g_{ds2} + g_{ds4})}{C_I} \quad (1)$$

$$\text{Output: } p_2 = \frac{-(g_{ds6} + g_{ds7})}{C_{II}} \quad (2) \quad C_{II} = C_L + C_{GD6} + C_{GD7}$$

- The frequency response is:  $A_v(s) = \frac{A_v(0)}{\left( \frac{s}{p_1} + 1 \right) \left( \frac{s}{p_2} + 1 \right)}$



$$v_{out}(t) = A_v(0) V_{in} \left[ 1 + \frac{p_2 e^{-tp_1}}{p_1 - p_2} - \frac{p_1 e^{-tp_2}}{p_1 - p_2} \right]$$


The time response at step input for small-signal (slew-rate not occurred)



# Two-stage, open-loop comparators
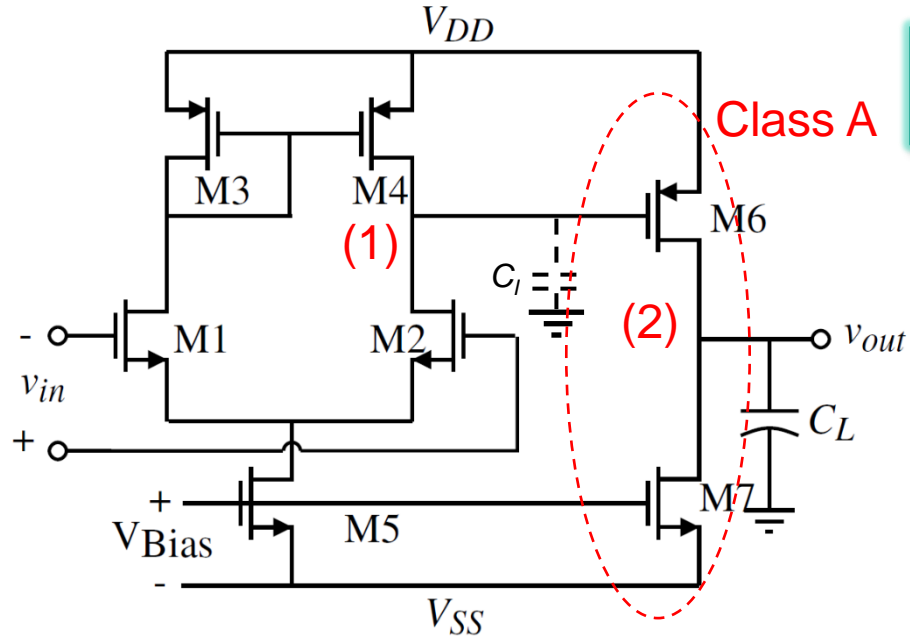
## Propagation delay time

- Assuming that the slew-rate does not occur



$$v_{out}(t) = A_v(0)V_{in} \left[ 1 + \frac{p_2 e^{-tp_1}}{p_1 - p_2} - \frac{p_1 e^{-tp_2}}{p_1 - p_2} \right]$$

- We define  $m$  and  $t_n$
- $$m = \frac{p_2}{p_1} \neq 1 \quad \text{and} \quad t_n = tp_1 = \frac{t}{\tau_1}$$

$$v_{out}'(t_n) = \frac{v_{out}(t)}{A_v(0)V_{in}} = 1 - \frac{m}{m-1}e^{-t_n} + \frac{1}{m-1}e^{-mt_n}$$

- The propagation delay time reduce  $m > 1$  ( $p_2 \gg p_1$ )
- In case of slew-rate mode, the propagation delay are:


$$SR^- = I_7 / C_{II}$$

Negative slew-rate

$$SR^+ = (I_6 - I_7) / C_{II}$$

Positive slew-rate

Similar to a Class A

 

# Dynamic characteristics

## Single pole response


- The small-signal dynamics are characterized by the frequency response of comparator that are similar to the frequency response of a single-pole amplifier

$$A_v(s) = \frac{A_v(0)}{\frac{s}{\omega_c} + 1} = \frac{A_v(0)}{s\tau_c + 1}$$


- $A_v(0)$  is the dc gain

- $\omega_c = 1/\tau_c$  is the -3dB frequency of the single (dominant) pole

 - Step response:  $v_o(t) = A_v(0) [1 - e^{-t/\tau_c}] V_{in} \quad (1)$


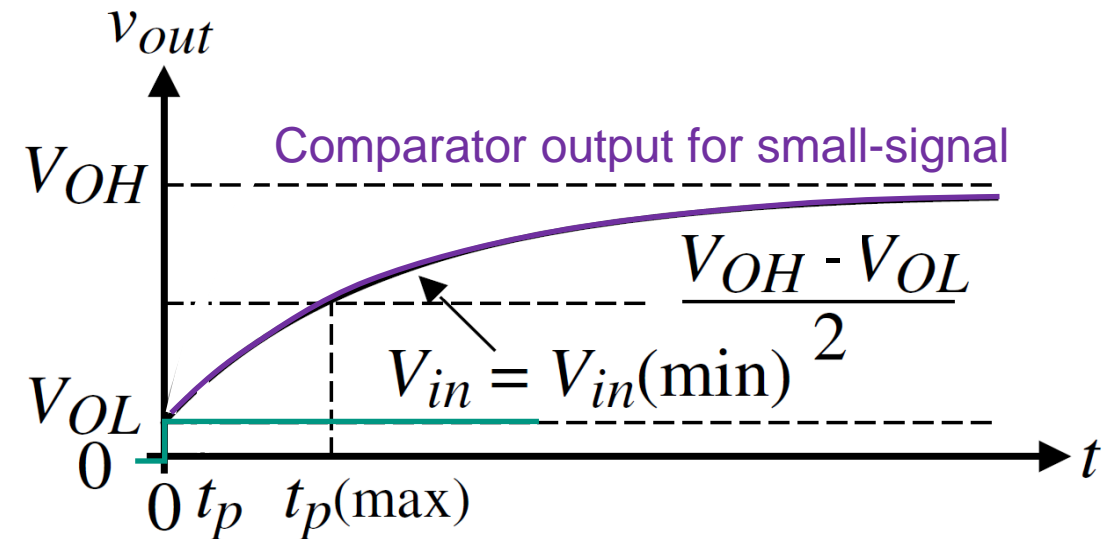
$$V_{in}(min) = \frac{V_{OH} - V_{OL}}{A_v(0)}$$




- The worst propagation delay  $t_p(max) \rightarrow$  when the  $V_{in}$  is close to the resolution of the comparator


# Comparators

*Comparators are divided in three classes*

High resolution

 

High speed

 

High speed  
and  
High resolution

High voltage gain amplification

- $A_v = \text{very high}$



Very low propagation delay

- Bandwidth = very high
- Circuit based on positive feedback
 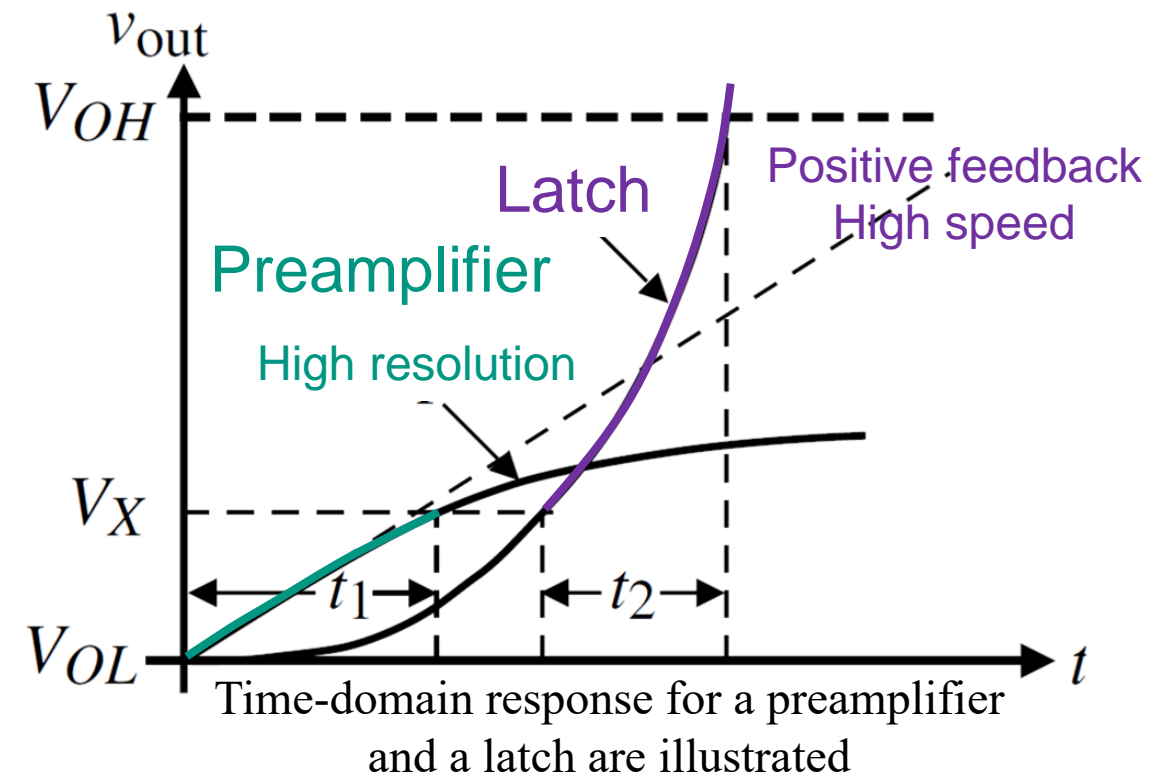
# High-speed Comparators

*Very fast comparator and very high resolution*


- A high-speed comparator should have a propagation delay time as small as possible
- By separating the comparator into a number of cascaded stages with a gain of  $A_0$  and a single pole at  $1/\tau$  (very high-frequency)
- The basic principle behind the high-speed comparator is to use a **preamplifier** to build up the input change to a sufficiently large value ( $V_X$ ) and then apply it to the **latch**. This combines the best aspects of circuits with a negative exponential response (the preamplifier) with circuits with a positive exponential response (the latch). **Total response time is  $t_1 + t_2$**
- Only preamplifier: the transition from  $V_{OL}$  to  $V_{OH}$  longer than  $t_1 + t_2$
- Only latch: would require longer time if the input is small



# High-speed Comparators
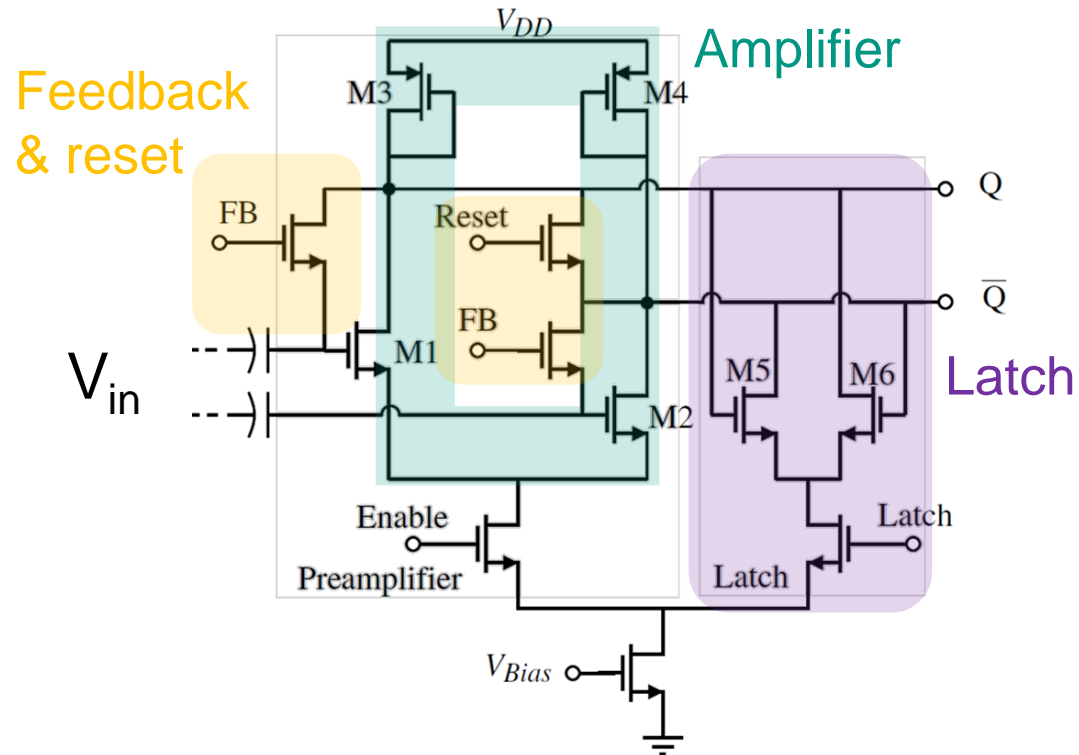
## High-speed comparators, circuit implementation

- The low-gain preamplifiers must compromise between a high bandwidth and sufficient gain



# High-speed Comparators

## High-speed comparators, circuit implementation


- The low-gain preamplifiers must compromise between a high bandwidth and sufficient gain

- Gain:  $A_v = -g_{m1}/g_{m3} = -g_{m2}/g_{m4} = -\sqrt{\frac{K_{N'}(W_1/L_1)}{K_{P'}(W_3/L_3)}}$

- Dominant pole:  $p_{\text{dominat}} = -g_{m3}/C = -g_{m4}/C$ , where  $C$  is the total capacitance at the node  $P$

- Advantage*: high-frequency


- Working principle ...

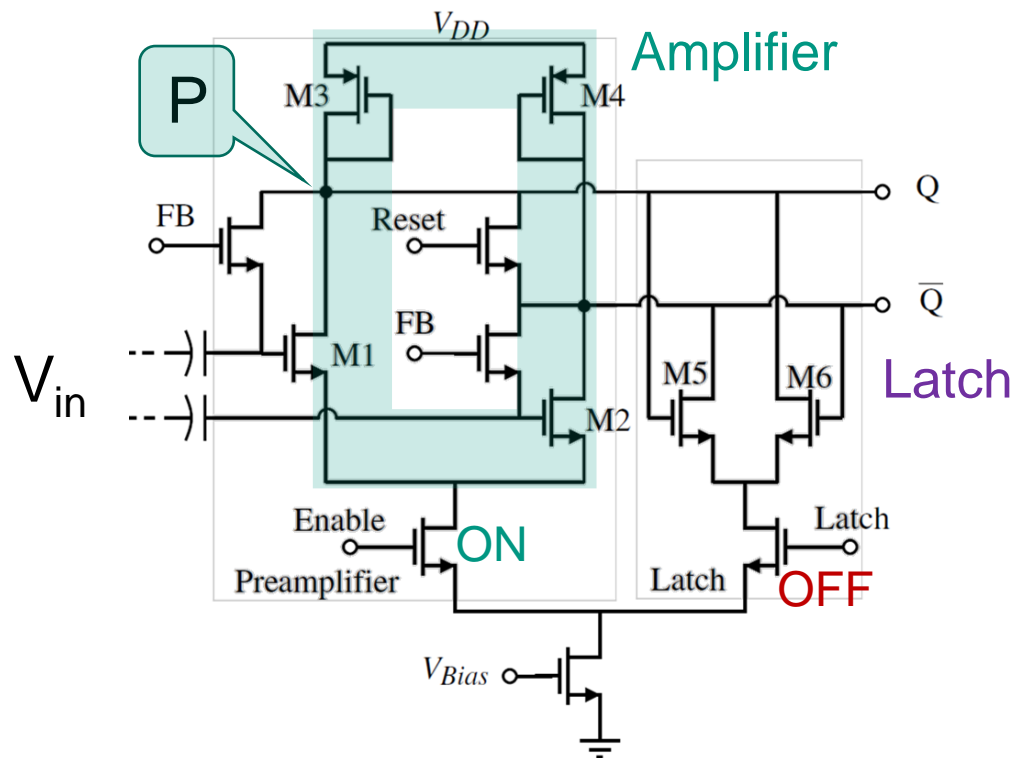

# High-speed Comparators
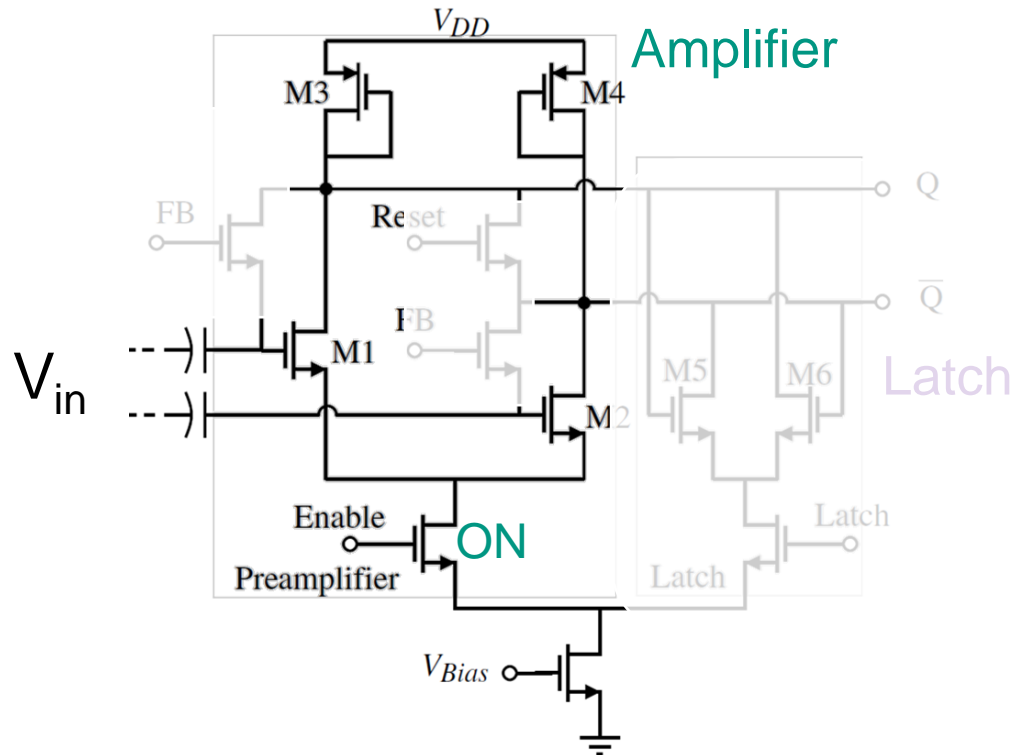
## High-speed comparators, circuit implementation

- The low-gain preamplifiers must compromise between a high bandwidth and sufficient gain




- **Step 1:** Enable Preamplifier = 1  $\rightarrow$  differential stage biased by  $V_{bias}$  MOS
- **Step 2:** Reset mode (FB = 1 & Reset = 1)  $\rightarrow Q = \bar{Q}$ , note that M1 and M2 are also connected in a diode mode by the FB and Reset MOS

# High-speed Comparators
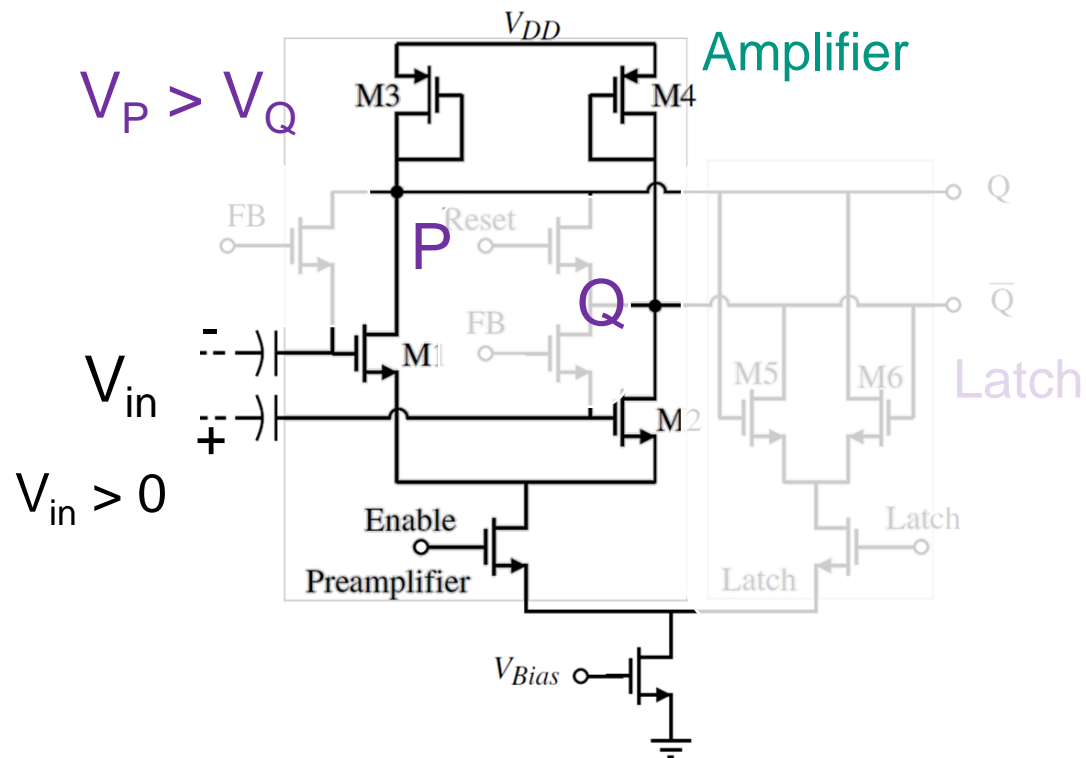
## High-speed comparators, circuit implementation

- The low-gain preamplifiers must compromise between a high bandwidth and sufficient gain




- **Step 1:** Enable Preamplifier = 1 → differential stage biased by  $V_{bias}$  MOS
- **Step 2:** Reset mode (FB = 1 & Reset = 1) →  $Q = \bar{Q}$ , note that M1 and M2 are also connected in a diode mode by the FB and Reset MOS
- **Step 3:** Preamp mode (FB = 0 & Reset = 0)  
 $V_{out\_preamp} = -A_V V_{in}$



# High-speed Comparators
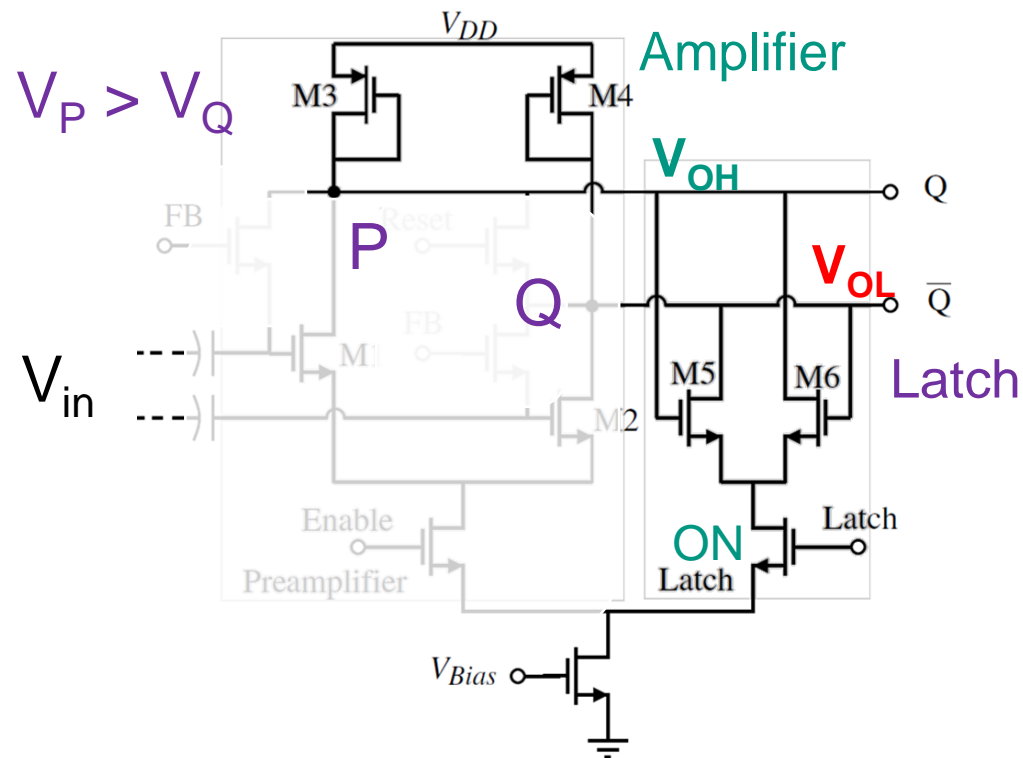
## High-speed comparators, circuit implementation


- The low-gain preamplifiers must compromise between a high bandwidth and sufficient gain



- **Step 1:** Enable Preamplifier = 1  $\rightarrow$  differential stage biased by  $V_{bias}$  MOS
- **Step 2:** Reset mode (FB = 1 & Reset = 1)  $\rightarrow$   $Q = \bar{Q}$ , note that M1 and M2 are also connected in a diode mode by the FB and Reset MOS
- **Step 3:** Preamp mode (FB = 0 & Reset = 0)  
 $V_{out\_preamp} = A_V V_{in}$
- **Step 4:** latch mode = 1 and Enable Preamplifier = 0, the positive feedback of the latch will set the final voltage levels  $V_{OH}$  and  $V_{OL}$
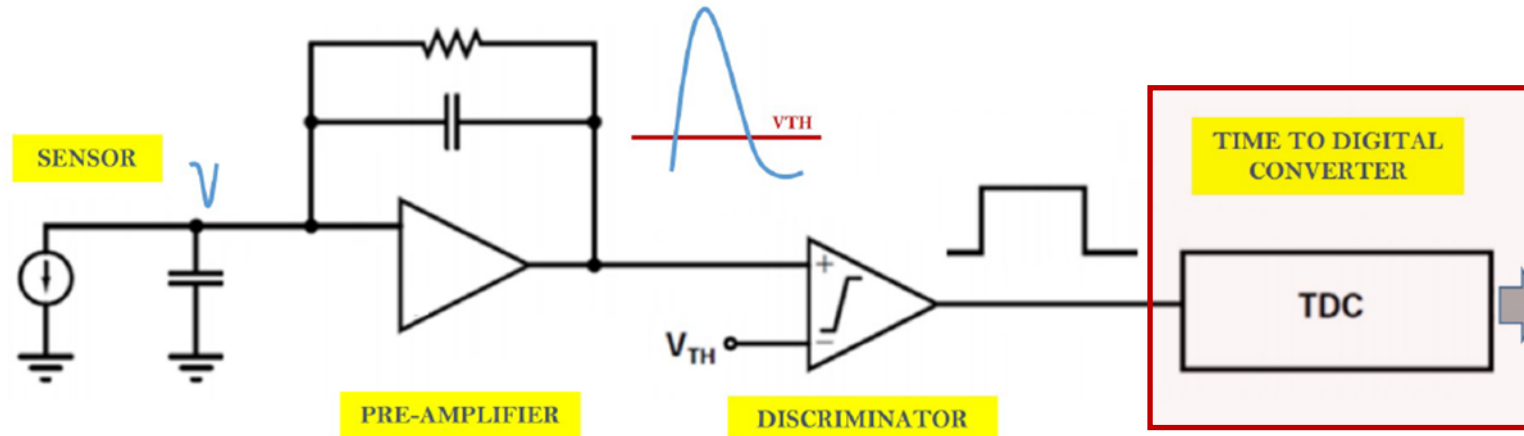
# Time resolution in timing detectors

The timing capabilities depends from the signal at the output of the pre-amplifier and by the TDC binning



$$\sigma_t^2 = \underbrace{\left(\frac{\text{Noise}}{dV/dt}\right)^2 + \sigma_{timewalk}^2}_{\text{Front-end}} + \underbrace{\left(\frac{\text{LSB}}{\sqrt{12}}\right)^2 + \sigma_{sensor}^2 + \sigma_{Landau}^2}_{\text{Sensor}} + \underbrace{\sigma_{TDC}^2}_{\text{TDC}}$$

**Total noise contribution**





TDC: Its contribution is negligible within the time resolution for  $\text{LSB} < 30 \text{ ps}$   
 It contributes with few ps of time jitter (uncertainty)

# Principle of COUNTER based TDC
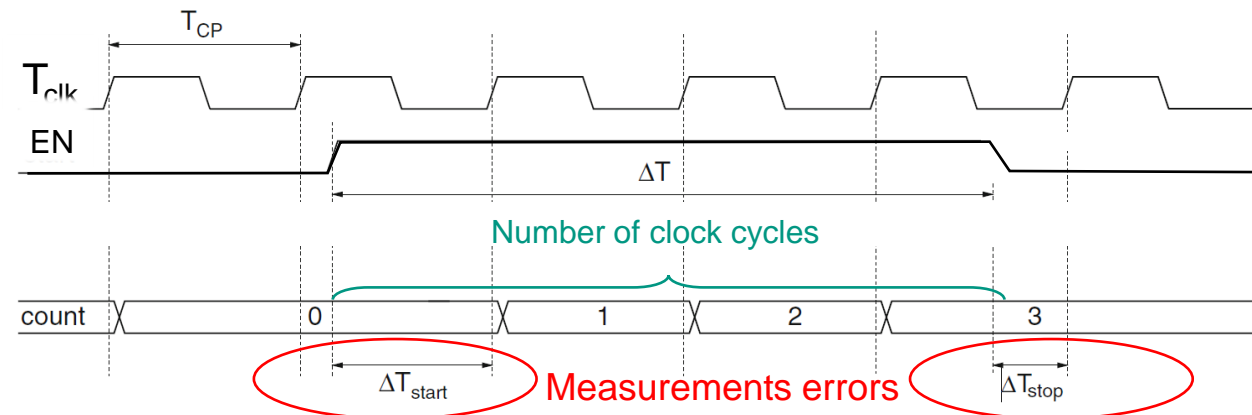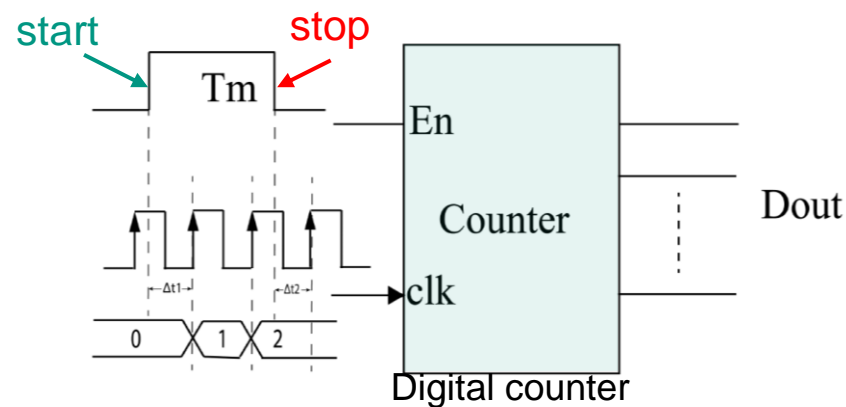
## The “first” TDC architecture

- Counter is the simplest and most reliable way of time measurement. The conceptual diagram of counter as TDC is as depicted in Figure, **the resolution depends on the frequency** of the clock input. The *advantages* of counter remains in its simplicity and reliability



- The simplest technique to **quantize a time interval is to count the cycles of a reference clock**. The measurement interval defined by the **start and stop signal is completely asynchronous to the reference clock signal** → this causes a measurement error  $\Delta T_{start}$  at the beginning and  $\Delta T_{stop}$  at the end of the time interval


- $$\Delta T = N \cdot T_{clk} + (T_{clk} - \Delta T_{stop}) - (T_{clk} - \Delta T_{start})$$

Quantization error  $\epsilon_T = \Delta T_{start} - \Delta T_{stop} \in [-T_{clk}; T_{clk}]$

# Delay line TDC – Second Generation
 
## FLASH - TDC architecture

- Delay line TDC is also called as *flash TDC*, *classical delay line TDC*, or *tapped delay line TDC*





- **Working principle:** delayed versions of the start signal are sampled on the rising edge of the stop signal, resulting in a thermometer code

# Delay line TDC – Second Generation
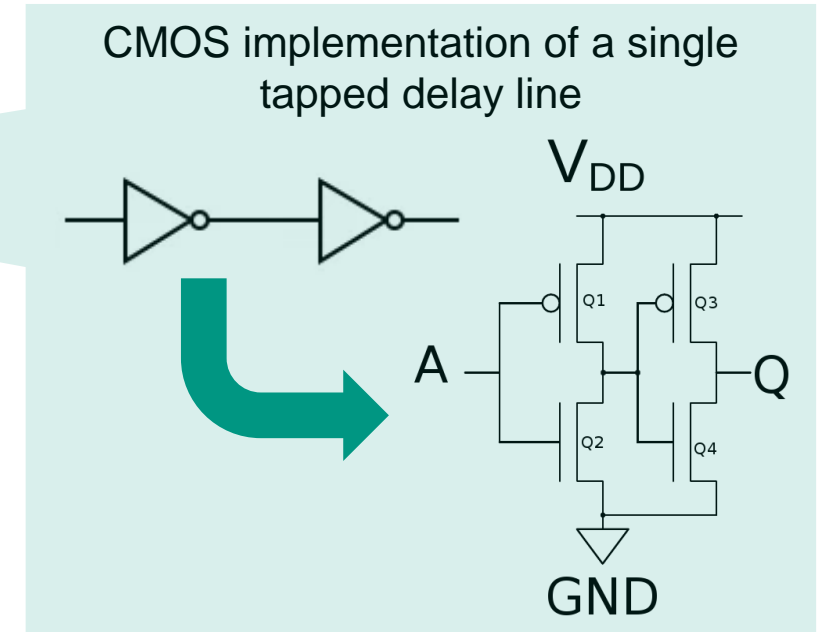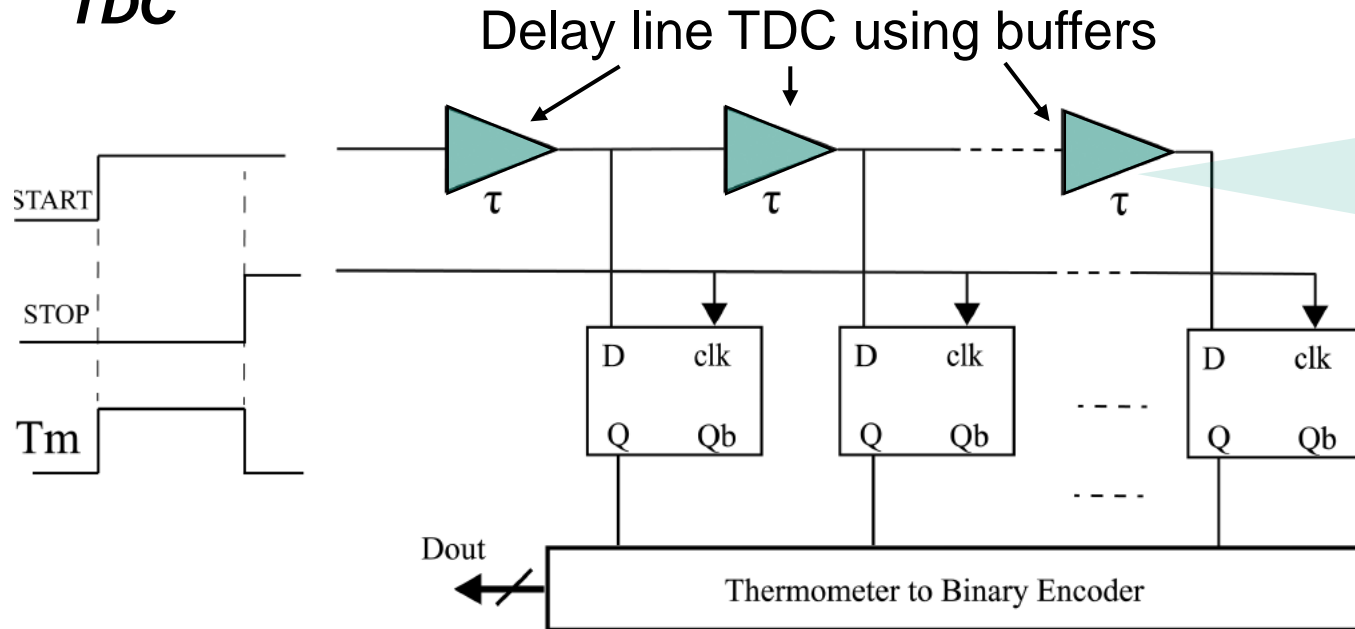
## FLASH - TDC architecture


- Delay line TDC is also called as *flash TDC*, *classical delay line TDC*, or *tapped delay line TDC*



- In both CMOS and FPGA technologies the resolution of the TDC is equal to the delay ( $\tau$ ) of the buffer
- The INL and DNL depends on the uniformity of the delays ( $\tau$ )

# Delay line TDC – Second Generation

## FLASH - TDC architecture

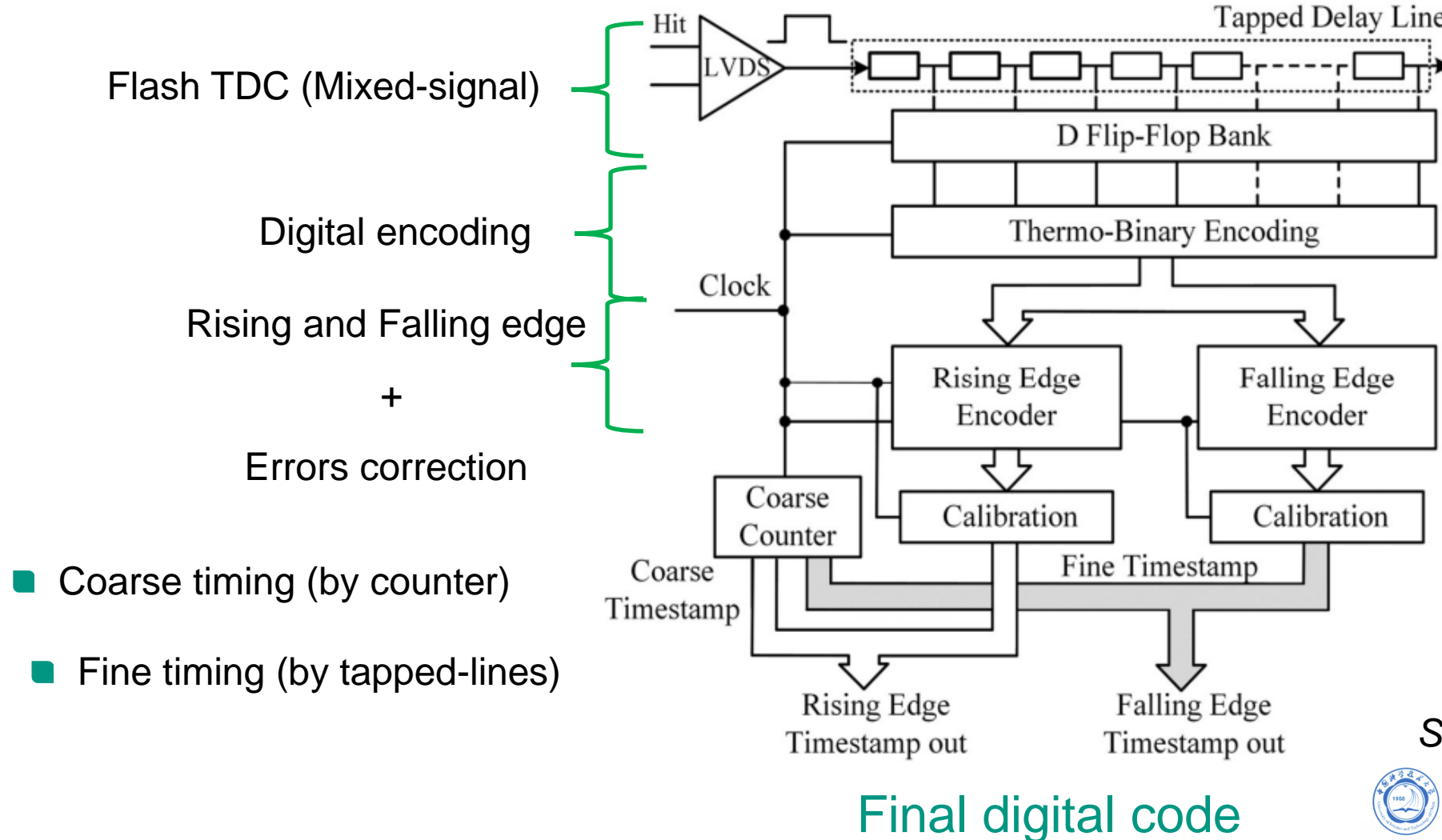


Source: Xinchu Xu



中国科学技术大学  
University of Science and Technology of China

# TDC resolution and quantization

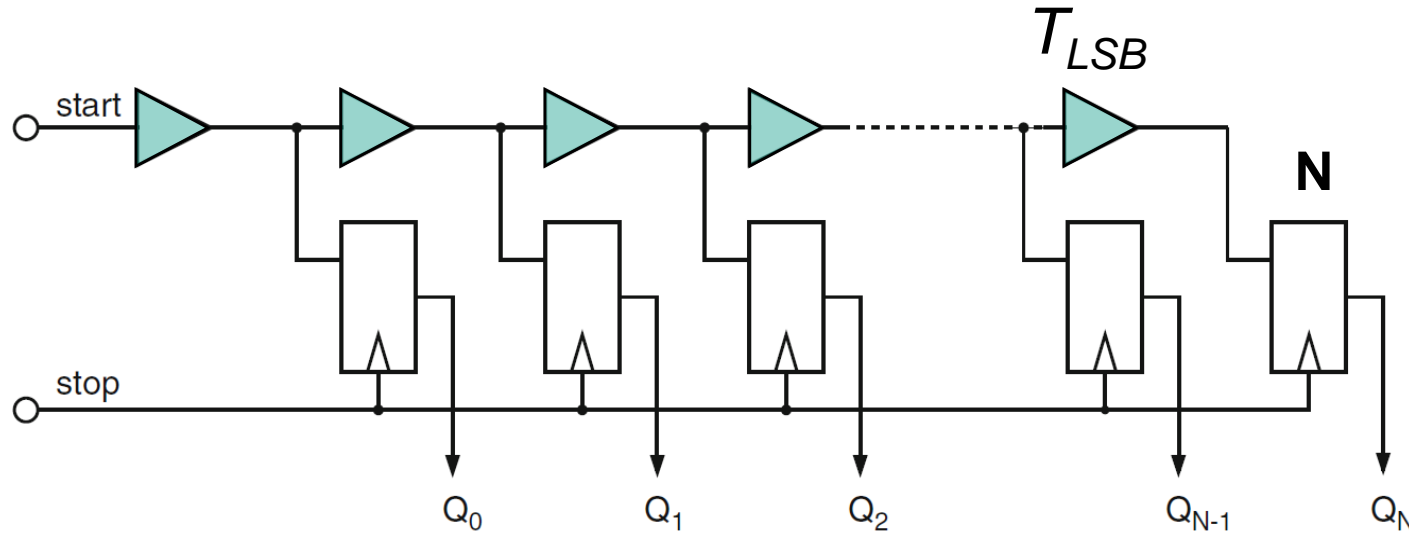


- The number  $N$  of all sampling elements with a HIGH output is related to the measurement interval  $\Delta T$  according to

$$N = \left\lfloor \frac{\Delta T}{T_{LSB}} \right\rfloor$$


- where  $T_{LSB}$  is the delay of a single delay element in the delay line
- The time interval  $\Delta T$  can be calculated from the number of HIGH outputs by  $\Delta T = N T_{LSB} + \epsilon$
- where  $\epsilon$  **describes the quantization error** that arises as a delay element has been either passed by the start signal yet or not

# Inverter Based Time-to-Digital Converter

## Inverter vs buffer

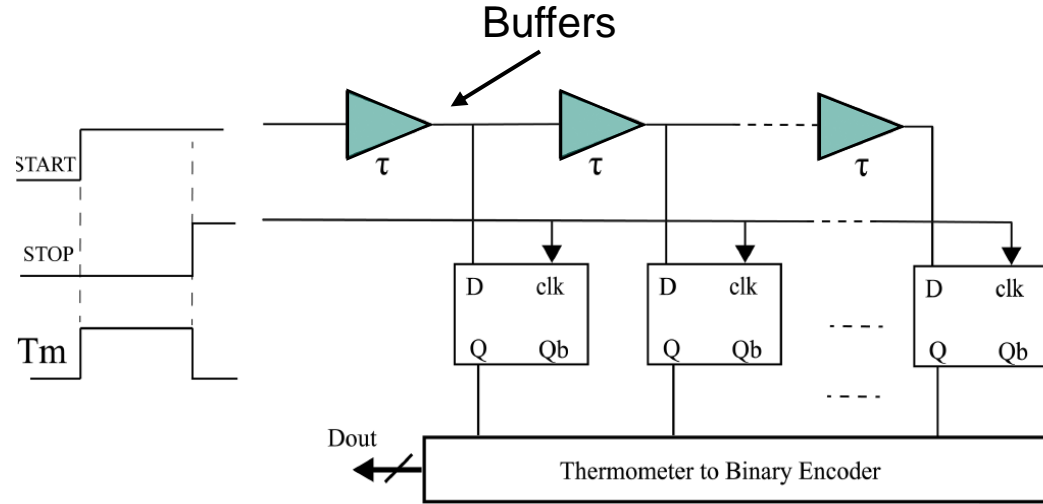

Buffer based TDC architecture

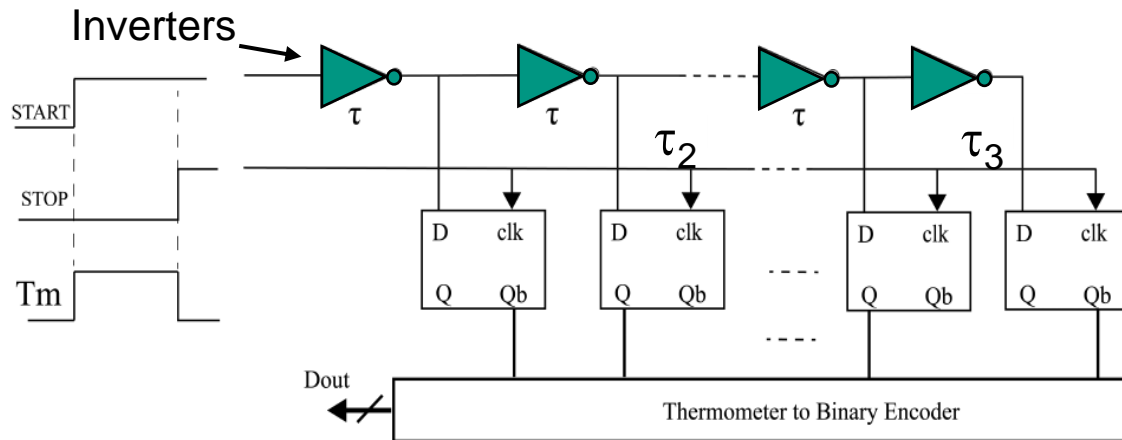

Delay based TDC architecture

- Replace buffer (two cascaded inverters) with inverter → doubles the resolution but reduces the dynamic range by half
- The thermometer code at the outputs of the sampling elements becomes a pseudo thermometer code with alternating ones and zeros:

1111111111111111 0000000000000000      buffer TDC  
 010101010101010 010101010101010      inverter TDC

- The length of the measurement interval is indicated not by a HIGH-LOW transition but by a phase change of the alternation HIGH-LOW sequence



# Time-to-Digital Converters – Third Generation

## TDC with Sub-Gate delay Resolution

- The resolution of time-to-digital converters is **limited by technology to one inverter delay**. Higher resolution can be achieved only by a faster technology.
- **What are the circuit techniques that allow to reach higher resolution TDC?** Thereby, do not depend on a single absolute gate delay
- The ratio between the **technology resolution** and the **actual resolution** is the so called **sub-gate delay interpolation factor IF**:

$$IF := \frac{T_{tech}}{T_{LSB}}$$

- TDCs with sub-gate delay resolution use sophisticated circuit techniques (resolution enhancement techniques) to circumvent the limitation of the technology delay




One method is Parallel Scaled Delay Elements

# Vernier TDC
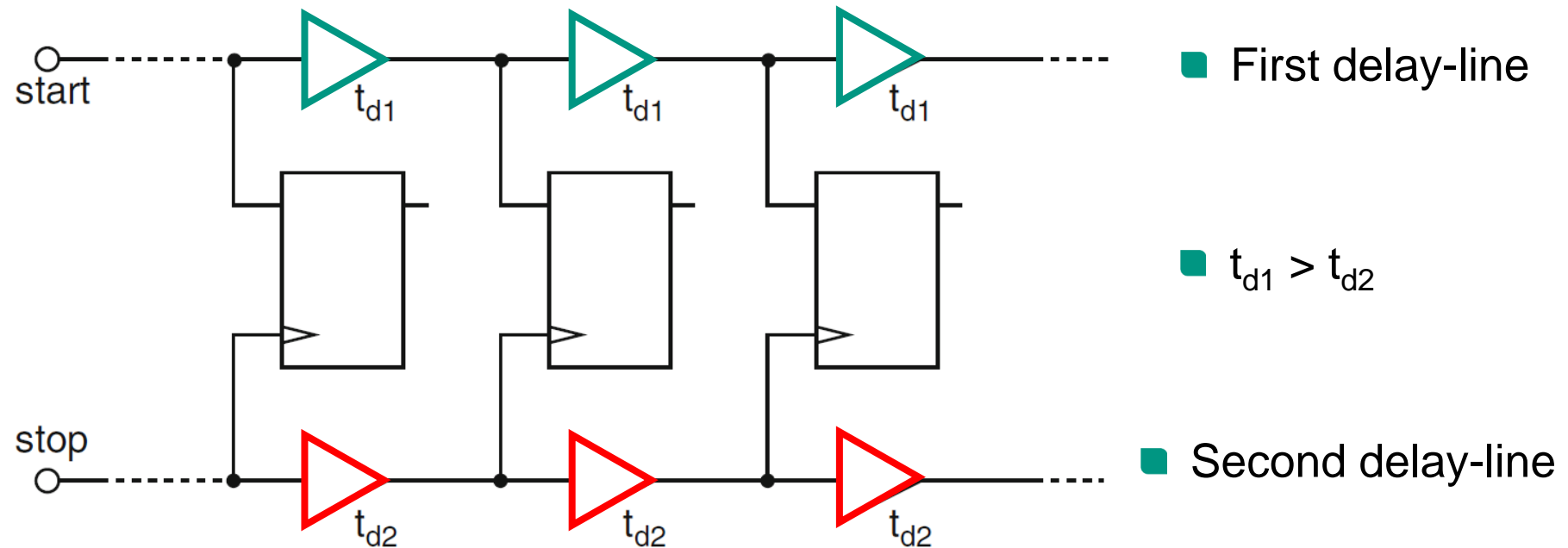
## Advanced Sub-Gate delay Resolution



- A delay-line based TDC that is capable of measuring time intervals with a sub-gate delay resolution is the Vernier TDC



- Cut-out of a Vernier TDC is based on a first delay-line for the start signal and a second one for the stop signal. The arrival time at two corresponding nodes is assessed by early-late detectors such as flip-flops

# Vernier TDC – working principle

## Advanced Sub-Gate delay Resolution

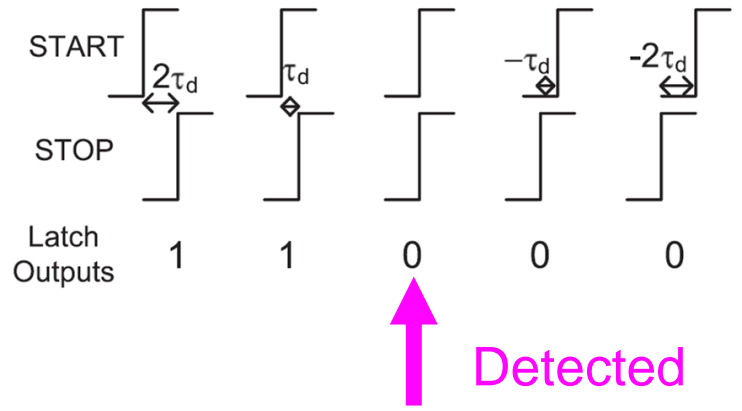
 


■ Thermometer code: 11 0000...

- Step 1: start signal propagates along the first delay-line.
- Step 2: stop signal occurs later, but the delays seen by this signal are smaller
- Step 3: The stop signal chases the start signal
- Step 4: The point (stage) where both signals are in phase is detected by early late detectors (ELDs), usually implemented as flip-flops
- The number of cells necessary for **STOP** signal to surpass the **START** signal represents the result of TDC conversion

# Vernier TDC – working principle

## Advanced Sub-Gate delay Resolution

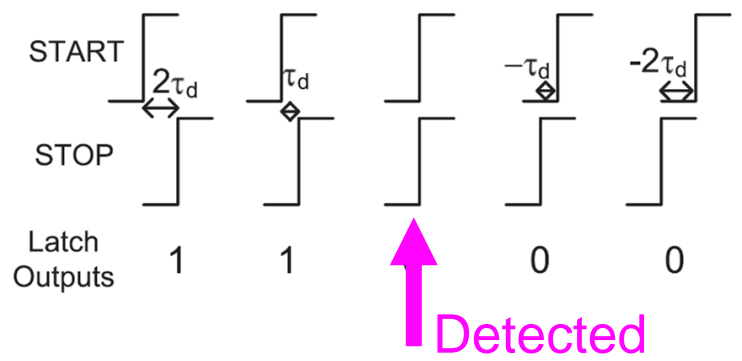 

- The granularity in the time domain, i.e. the TDC resolution, is the delay difference  $T_{LSB} = t_{d1} - t_{d2}$  between the elements in the delay-lines, **which can be made arbitrarily small**, therefore **the resolution does not depend on a gate delay**, but on the difference of two gate delays. Consequently, the Vernier TDC provides a circuit technique to overcome the resolution limitations given by a certain technology
- The price for this increased resolution is: the area, the power consumption and the latency. Because the skew between the signals in the first and the second delay line is reduced by  $T_{LSB}$  in each stage, a maximum number of  $N$  stages required to measure a maximum time interval  $T_{max}$  is

$$N = \frac{T_{max}}{T_{LSB}} = \frac{T_{max}}{t_{d1} - t_{d2}}$$

$$A_{core}^{Vernier} = \frac{T_{max}}{T_{LSB}} (4A^{inv} + A^{FF})$$


$A^{inv}$  = area of one inverter and  
 $A^{FF}$  = area of one flip-flop

TDC Power consumption  $0,4 \text{ mA} * 1.2\text{V} = 0,5 \text{ mW} @ 10\% \text{ occupancy}$


## TOA TDC

- Resolution: 20 ps
- Range: 2.5 ns
- 7 bits

@ Bojan Markovic, SLAC

 


## Simplified Block Diagram:

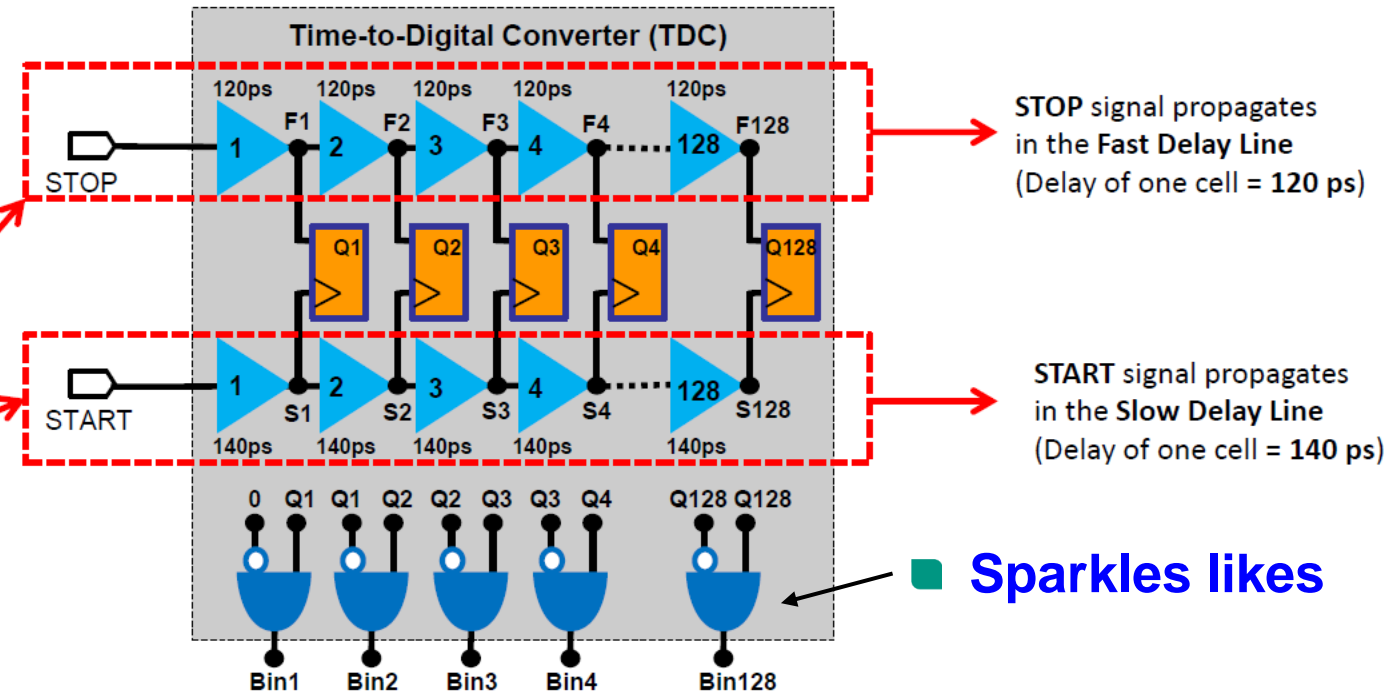

Differential shunt capacitor voltage-controlled delay cells

- The **START** pulse comes first and initializes the TDC operation.
- The **STOP** pulse follows the **START** with a delay that represents the time interval to be digitalized.
- At each tap of the Delay Line the **STOP** signal catches up to the **START** signal by the difference of the propagation delays of cells in Slow and Fast branches of the delay line: i.e.  $140\text{ps} - 120\text{ps} = 20\text{ps}$  that represents the **LSB** of time measurement.
- The number of cells necessary for **STOP** signal to surpass the **START** signal represents the result of TDC conversion
- Cycling configuration used in order to reduce the total number of Delay Cells.
- TDC range is equal to  $128 * 20\text{ps} = 2.56\text{ns}$

 

Thank you so much for  
your kind attention!

[michele.caselle@kit.edu](mailto:michele.caselle@kit.edu)